

Outline

- Introduction – *“Is there a limit?”*
- Transistors – *“CMOS building blocks”*
- Parasitics – *“The [un]desirables”*
- The CMOS inverter – *“A masterpiece”*
- Gates – *“Just like LEGO”*
- Sequential circuits – *“Time also counts!”*
- Storage elements – *“A bit in memory”*
- Technology scaling – *“..., faster!”*
- Technology – *“Building an inverter”*


“The [un]desirables”

- Delay in CMOS circuits
- MOSFET capacitances:
 - Physical structure
 - Channel
 - p-n junctions
- MOS resistances
- MOS equivalent circuit

What causes delay?


- In MOS circuits capacitive loading is the main cause
- Due to:
 - Device capacitance
 - Interconnect capacitance
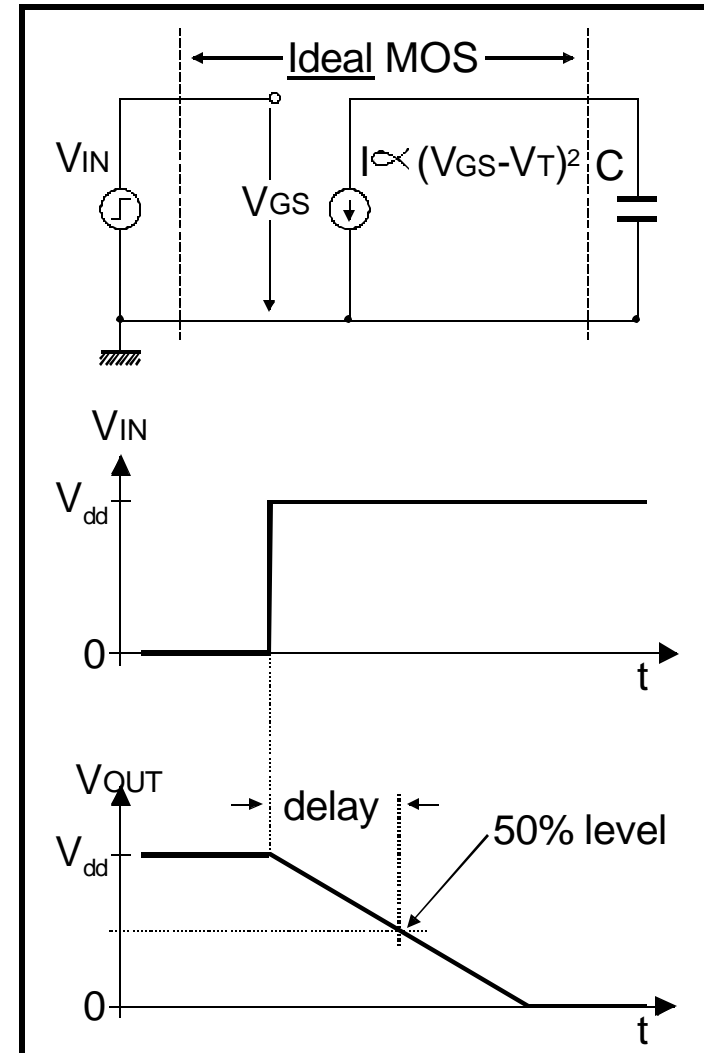
$$\Delta t = C \cdot \frac{\Delta V}{I} \approx \frac{C}{2 \cdot m \cdot C_{ox} \cdot V_{dd}} \cdot \frac{L}{W}$$



MOSFET capacitances

 - MOS capacitances have three origins:
 - The basic MOS structure
 - The channel charge
 - The pn-junctions depletion regions



MOS structure capacitances


- Source/drain diffusion extend below the gate oxide by:
 - x_d - the lateral diffusion
- This gives origin to the source/drain overlap capacitances:

$$C_{gso} = C_{gdo} = C_o \times W$$

$$C_o \text{ (F / m)}$$

- Gate-bulk overlap capacitance:
 
$$C_{gbo} = C'_o \times L, \quad C'_o \text{ (F / m)}$$



MOS structure capacitances

0.24 μm process

NMOS

$L(\text{drawn}) = 0.24 \mu\text{m}$

$L(\text{effective}) = 0.18 \mu\text{m}$

$W(\text{drawn}) = 2 \mu\text{m}$

$C_o (s, d, b) = 0.36 \text{ fF}/\mu\text{m}$

$C_{\text{ox}} = 5.6 \text{ fF}/\mu\text{m}^2$

$C_{\text{gso}} = C_{\text{gdo}} = 0.72 \text{ fF}$

$C_{\text{gbo}} = 0.086 \text{ fF}$


$C_g = 2.02 \text{ fF}$

Channel capacitance

- The channel capacitance is nonlinear
- Its value depends on the operation region
- Its formed of three components:
 - C_{gb} - gate-to-bulk capacitance
 - C_{gs} - gate-to-source capacitance
 - C_{gd} - gate-to-drain capacitance

| <i>Operation region</i> | C_{gb} | C_{gs} | C_{gd} |
|-------------------------|--------------|--------------------|--------------------|
| Cutoff | $C_{ox} W L$ | 0 | 0 |
| Linear | 0 | $(1/2) C_{ox} W L$ | $(1/2) C_{ox} W L$ |
| Saturation | 0 | $(2/3) C_{ox} W L$ | 0 |

Channel capacitance

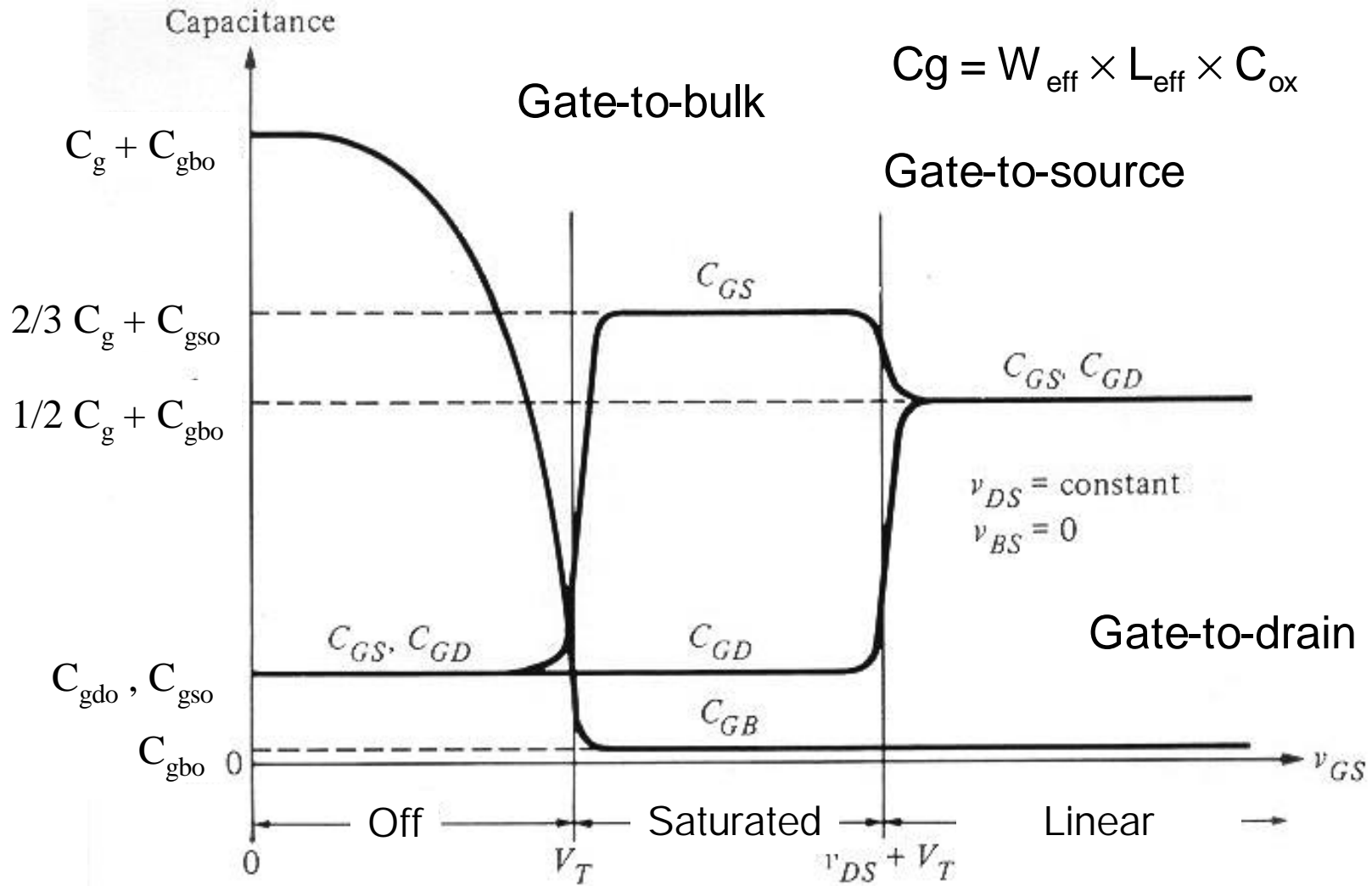


Junction capacitances

- C_{sb} and C_{db} and diffusion capacitances composed of:
 - Bottom-plate capacitance:

$$C_{bottom} = C_j \cdot W \cdot L_s$$

- Side-wall capacitance:

$$C_{sw} = C_{jsw} \cdot (2L_s + W)$$

 

Junction capacitances

0.24 μm process

NMOS

$L(\text{drawn}) = 0.24 \mu\text{m}$

$L(\text{effective}) = 0.18 \mu\text{m}$

$W(\text{drawn}) = 2 \mu\text{m}$

$L_s = 0.8 \mu\text{m}$

$C_j(s, d) = 1.05 \text{ fF}/\mu\text{m}^2$

$C_{j\text{sw}} = 0.09 \text{ fF}/\mu\text{m}$

$C_{\text{bottom}} = 1.68 \text{ fF}$

$C_{\text{sw}} = 0.32 \text{ fF}$


$C_g = 2.02 \text{ fF}$

Source/drain resistance

- Scaled down devices \Rightarrow higher source/drain resistance:

$$R_{s,d} = \frac{L_{s,d}}{W} \cdot R_{sq} + R_c$$

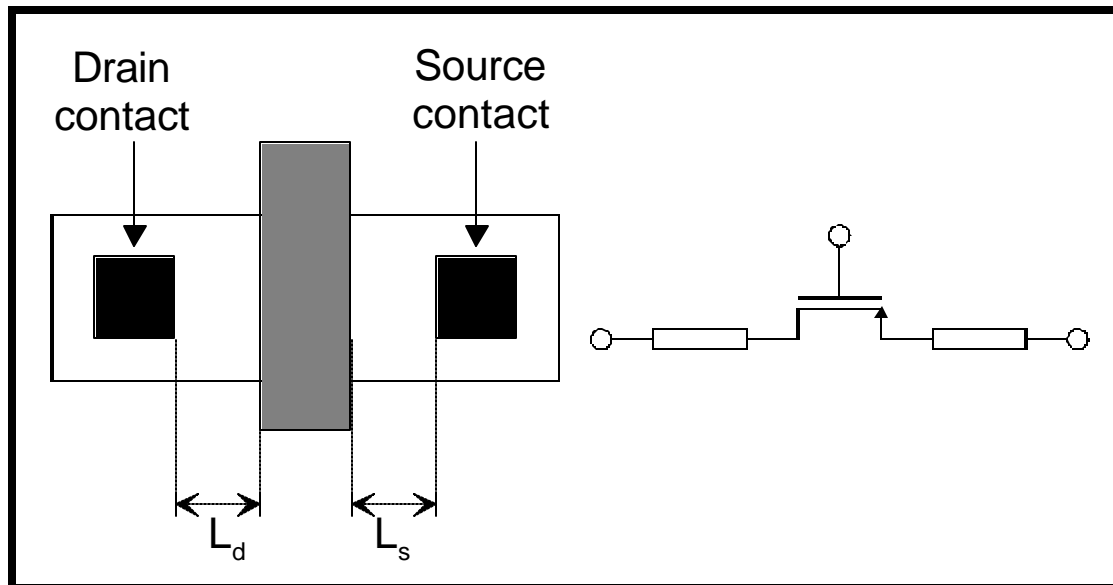- In sub- μ processes silicidation is used to reduce the source, drain and gate parasitic resistance




0.24 μm process

$R(P+) = 4 \Omega/\text{sq}$

$R(N-) = 4 \Omega/\text{sq}$

MOSFET model

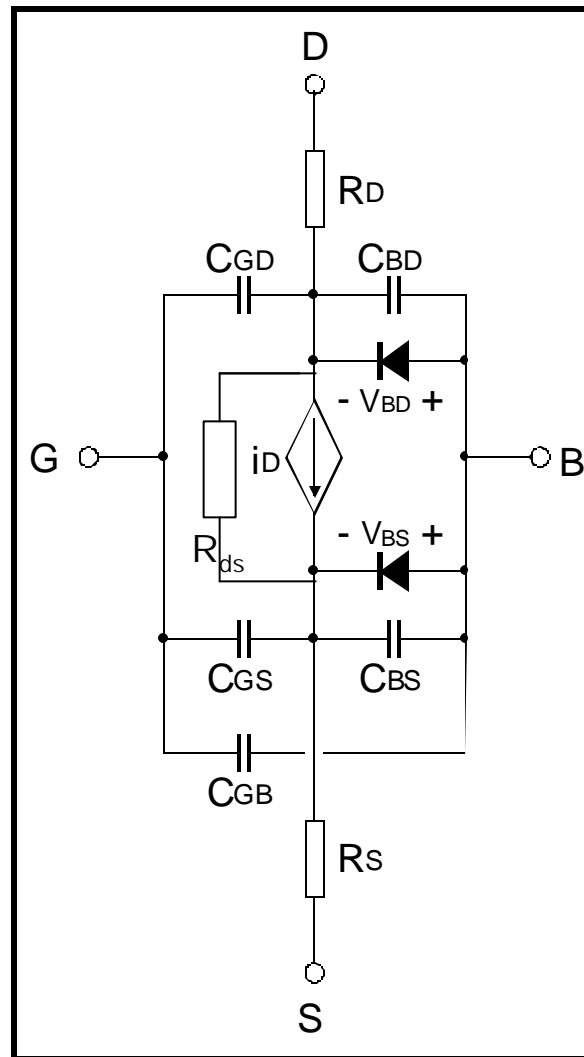

Outline


- Introduction – *“Is there a limit?”*
- Transistors – *“CMOS building blocks”*
- Parasitics – *“The [un]desirables”*
- **The CMOS inverter – *“A masterpiece”***
- Gates – *“Just like LEGO”*
- Sequential circuits – *“Time also counts!”*
- Storage elements – *“A bit in memory”*
- Technology scaling – *“..., faster!”*
- Technology – *“Building an inverter”*

“A masterpiece”

- Logic levels
- MOST – a simple switch
- The CMOS inverter:
 - DC operation
 - Dynamic operation
 - Propagation delay
 - Power consumption
 - Layout



CMOS logic: "0" and "1"

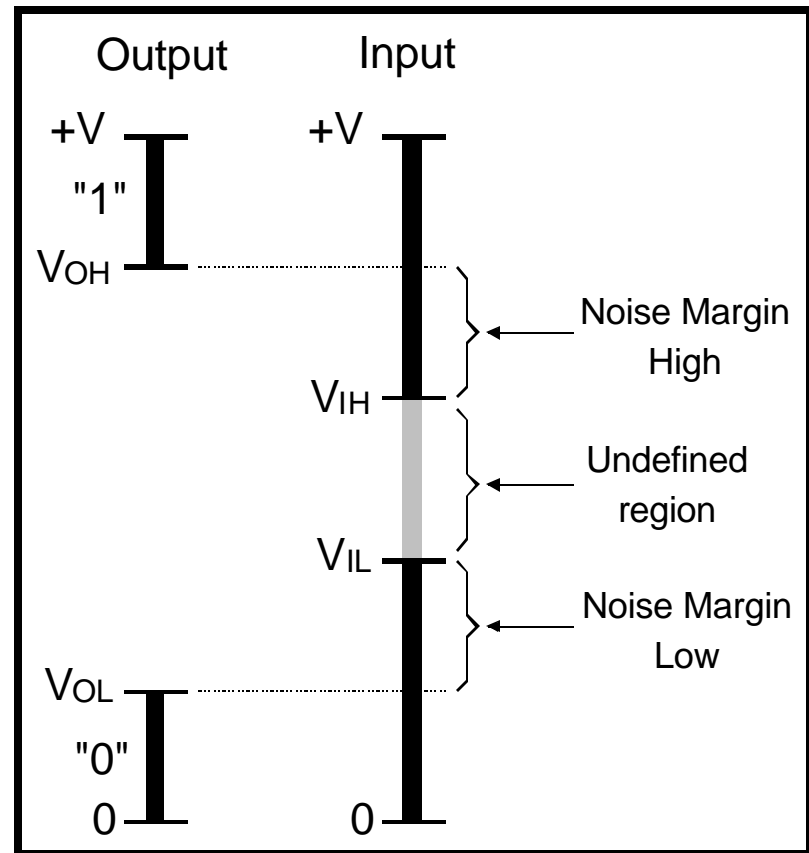- Logic circuits process Boolean variables
- Logic values are associated with voltage levels:
 - $V_{IN} > V_{IH} \Rightarrow "1"$
 - $V_{IN} < V_{IL} \Rightarrow "0"$
- Noise margin:
 - $NM_H = V_{OH} - V_{IH}$
 - $NM_L = V_{IL} - V_{OL}$





The MOST - a simple switch

p-switch

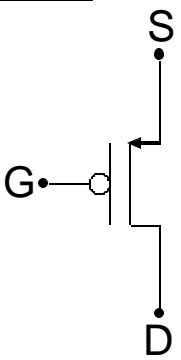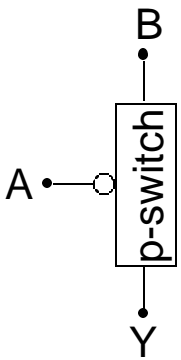
| A | B | Y |
|---|---|-------------------------|
| 0 | 0 | bad 0 (source follower) |
| 0 | 1 | good 1 |
| 1 | 0 | ? (high Z) |
| 1 | 1 | ? (high Z) |

n-switch

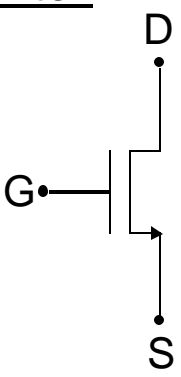
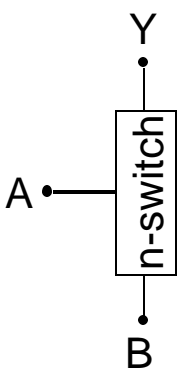



| A | B | Y |
|---|---|-------------------------|
| 0 | 0 | ? (high Z) |
| 0 | 1 | ? (high Z) |
| 1 | 0 | good 0 |
| 1 | 1 | bad 1 (source follower) |

The CMOS inverter

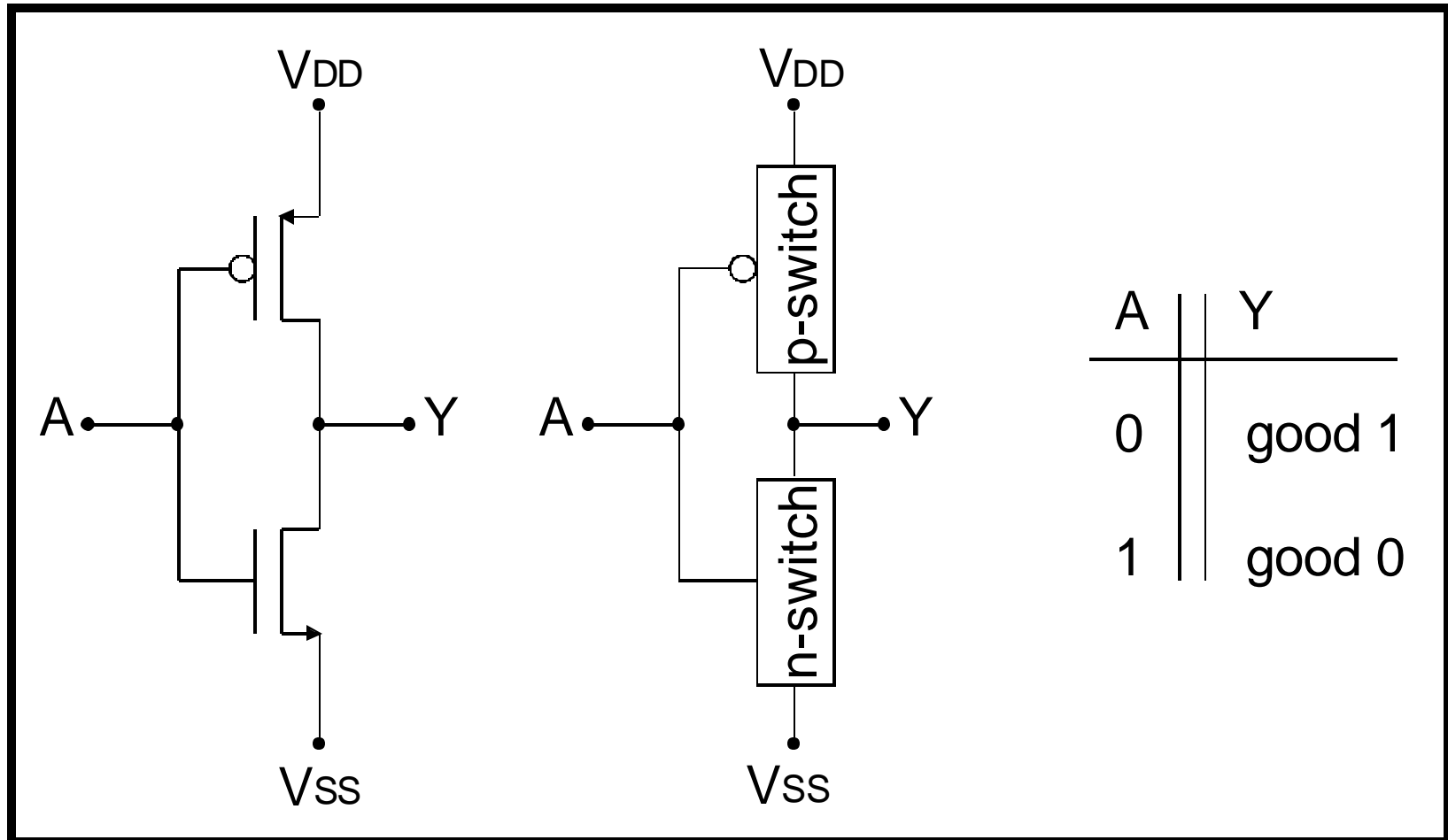

The CMOS inverter

  


The CMOS inverter

Regions of operation (balanced inverter):

| V_{in} | n-MOS | p-MOS | V_{out} |
|---|------------|------------|---------------|
| 0 | cut-off | linear | V_{dd} |
| $V_{TN} < V_{in} < V_{dd}/2$ | saturation | linear | $\sim V_{dd}$ |
| $V_{dd}/2$ | saturation | saturation | $V_{dd}/2$ |
| $V_{dd} - V_{TP} > V_{in} > V_{dd}/2$ | linear | saturation | ~ 0 |
| V_{dd} | linear | cut-off | 0 |

The CMOS inverter

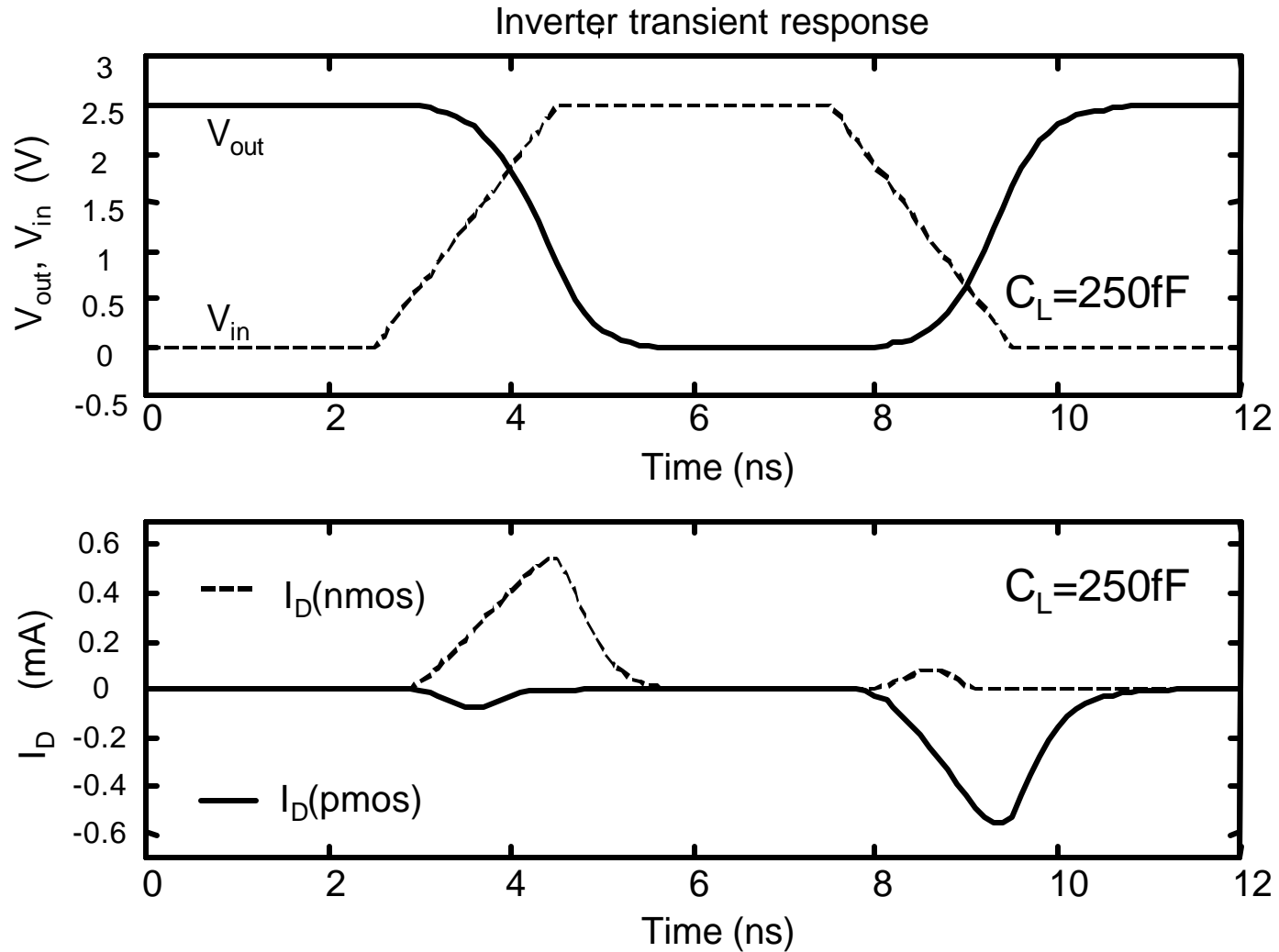

The CMOS inverter

- Propagation delay
 - Main origin: load capacitance

$$t_{pLH} = \frac{C_L \cdot V_{dd}}{k_p (V_{dd} - |V_{TP}|)^2} \approx \frac{C_L}{k_p \cdot V_{dd}}$$

$$t_{pHL} = \frac{C_L \cdot V_{dd}}{k_n (V_{dd} - |V_{TN}|)^2} \approx \frac{C_L}{k_n \cdot V_{dd}}$$

$$t_p \approx \frac{1}{2} (t_{pLH} + t_{pHL}) = \frac{C_L}{2 \cdot V_{dd}} \left(\frac{1}{k_n} + \frac{1}{k_p} \right)$$


- To reduce the delay:
 - Reduce C_L
 - Increase k_n and k_p . That is, increase W/L

The CMOS inverter


- CMOS power budget:
 - Dynamic power consumption:
 - Charging and discharging of capacitors
 - Short circuit currents:
 - Short circuit path between power rails during switching
 - Leakage
 - Leaking diodes and transistors

The CMOS inverter

 
- The dynamic power dissipation is a function of:
 - Frequency
 - Capacitive loading
 - Voltage swing
- To reduce dynamic power dissipation
 - Reduce: C_L
 - Reduce: f
 - Reduce: $V_{dd} \Leftarrow$ The most effective action



The CMOS inverter

 

The CMOS inverter

 


Outline

- Introduction – *“Is there a limit?”*
- Transistors – *“CMOS building blocks”*
- Parasitics – *“The [un]desirables”*
- The CMOS inverter – *“A masterpiece”*
- **Gates – *“Just like LEGO”***
- Sequential circuits – *“Time also counts!”*
- Storage elements – *“A bit in memory”*
- Technology scaling – *“..., faster!”*
- Technology – *“Building an inverter”*

“Just like LEGO”


- The NAND gate
- “Reading” CMOS gates
- Designing CMOS gates

NAND 2-inputs

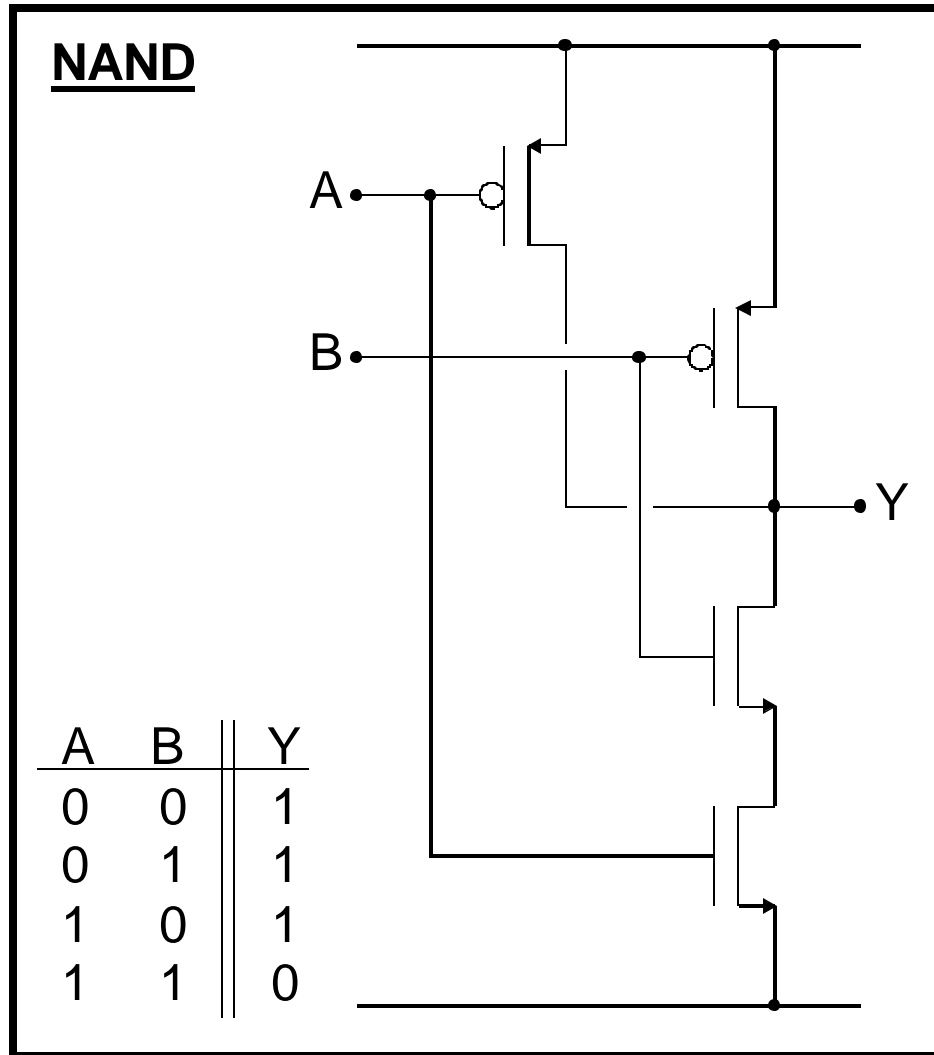


"Gates are inverters in disguise!"


NAND 3-inputs

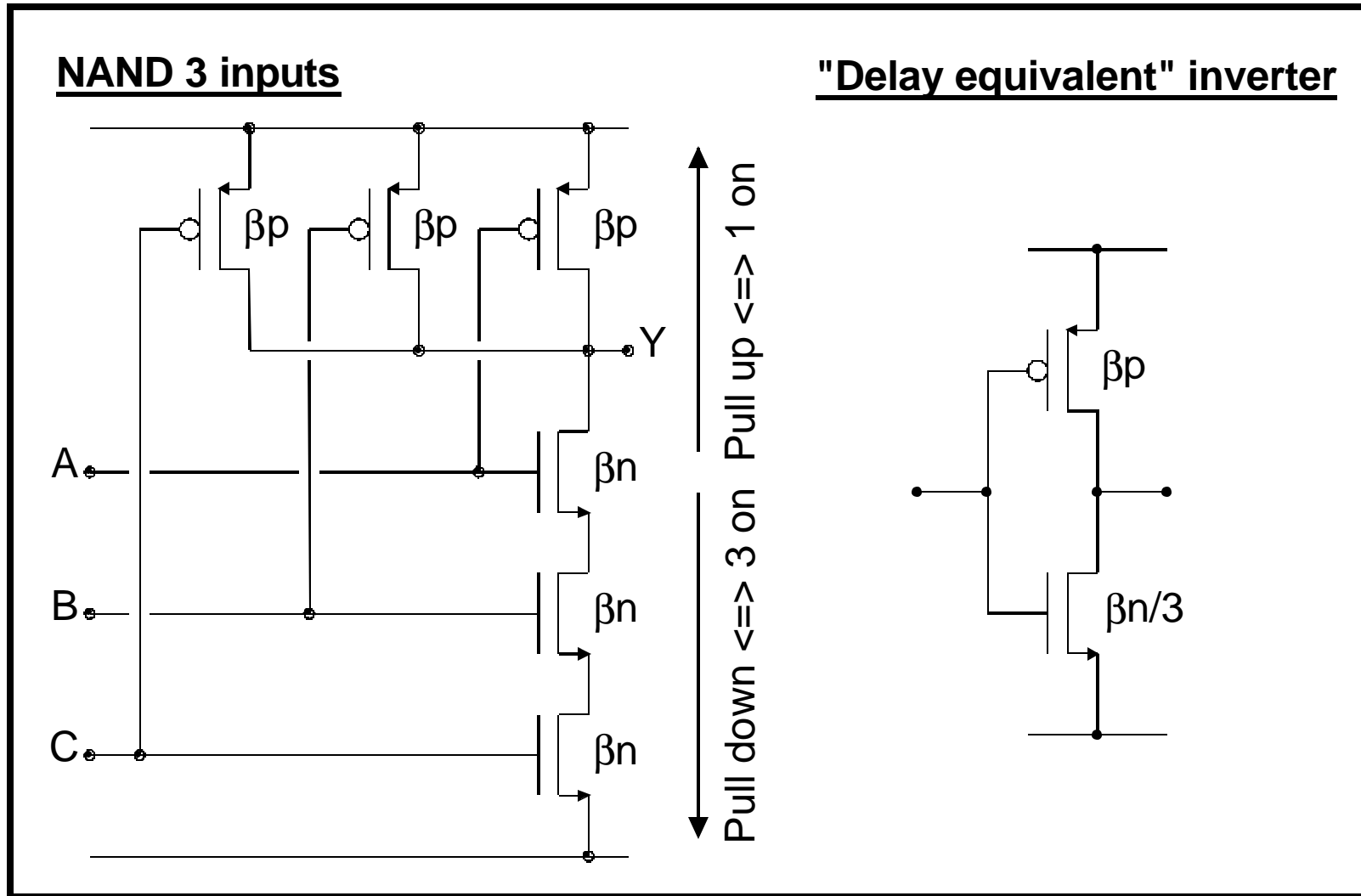


NAND 3-inputs

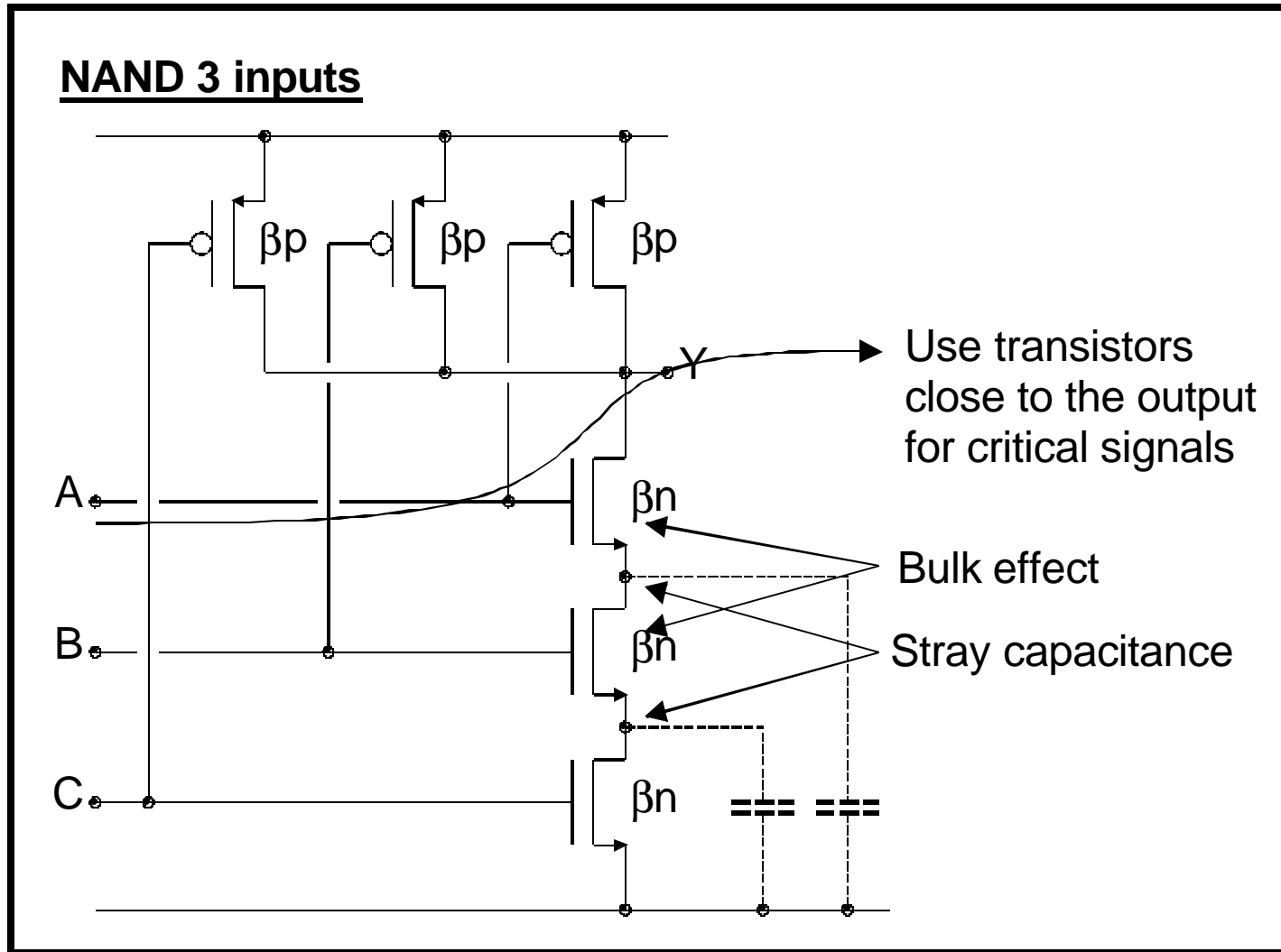


NAND 3-inputs

 


NAND 3-inputs

 

“Reading” CMOS gates

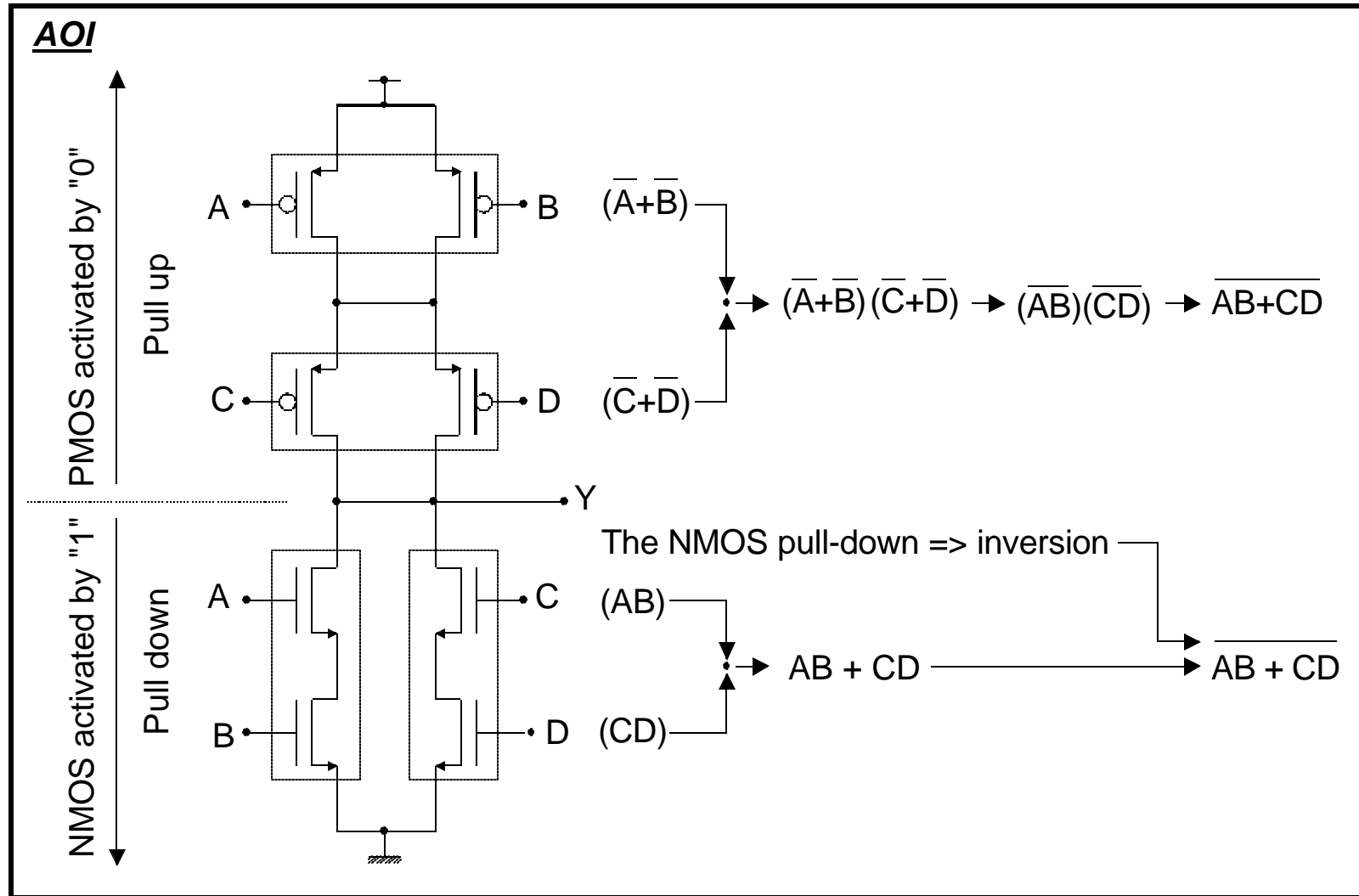

Designing CMOS gates

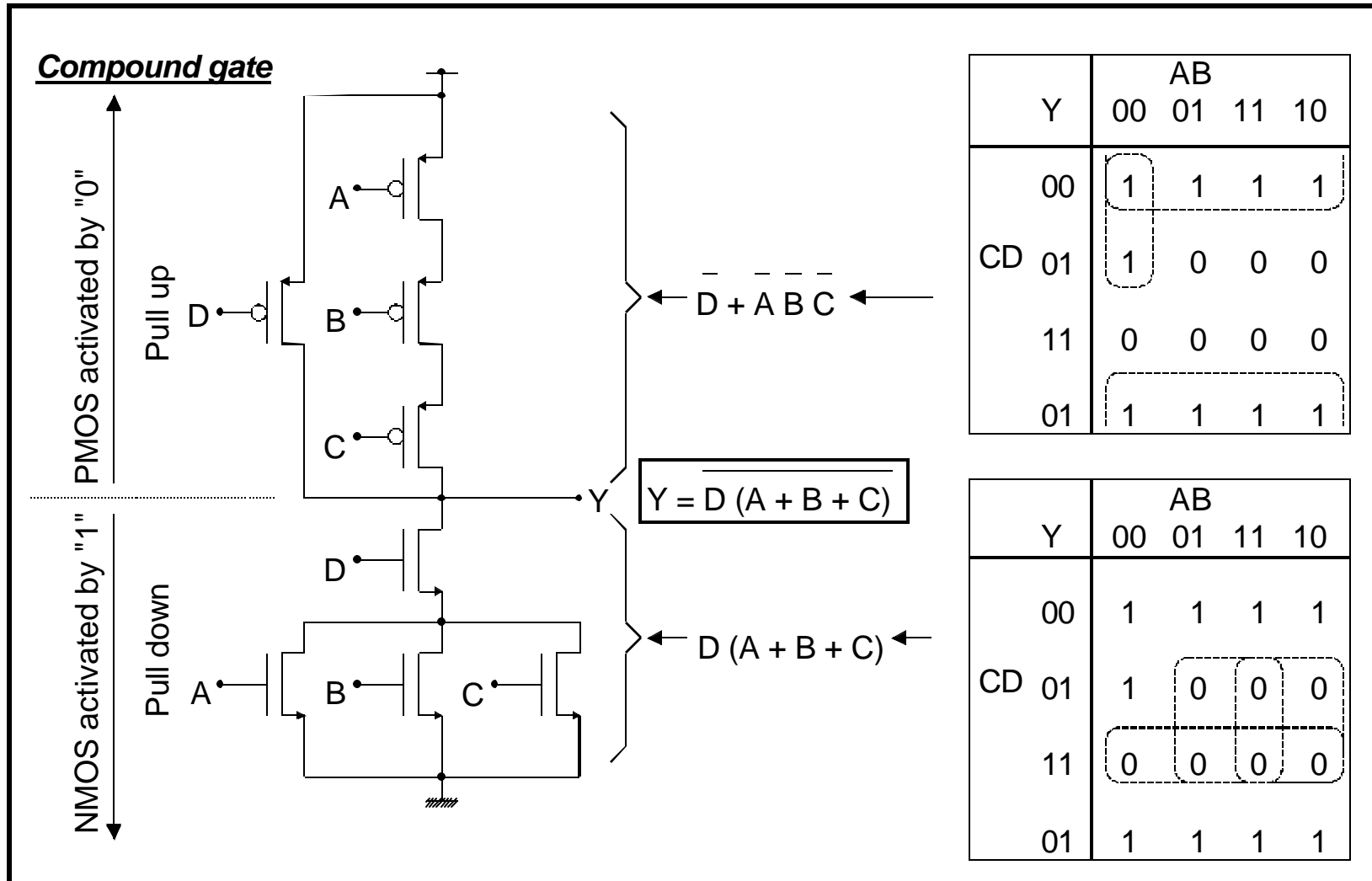

Complex CMOS gates

- Can a compound gate be arbitrarily complex?

- NO, propagation delay is a strong function of fan-in:

$$t_p = a_0 \cdot FO + a_1 \cdot FI + a_2 \cdot (FI)^2$$

- FO \Rightarrow Fan-out, number of loads connected to the gate:

- 2 gate capacitances per FO + interconnect

- FI \Rightarrow Fan-in, Number of inputs in the gate:

- Quadratic dependency on FI due to:
 - Resistance increase
 - Capacitance increase

- Avoid large FI gates (Typically $FI \leq 4$)