

Outline

- Introduction – *“Is there a limit?”*
- Transistors – *“CMOS building blocks”*
- Parasitics – *“The [un]desirables”*
- The CMOS inverter – *“A masterpiece”*
- Gates – *“Just like LEGO”*
- Sequential circuits – *“Time also counts!”*
- **Storage elements – *“A bit in memory”***
- Technology scaling – *“..., faster!”*
- Technology – *“Building an inverter”*

“A bit in memory”

Memory cells:


- Read-only
- Nonvolatile R/W
- Read-write
 - 6T SRAM
 - Resistive load SRAM
 - 3T dynamic
 - 1T dynamic

Storage elements

- The silicon area of large memory cells is dominated by the size of the memory core, it is thus crucial to keep the size of the basic storage cell as small as possible
- Reduced storage cell area results in:
 - reduced driving capability (small devices)
 - reduced logic swing and the noise margins
 - Consequently, sense amplifiers are necessary to restore full rail-to-rail amplitude


Read-only

- Because the contents is permanently fixed the cell design is simplified
- Upon activation of the word line a 0 or 1 is presented to the bit line:
 - If the NMOS is absent the word line has no influence on the bit line:
 - The word line is pulled-up by the resistor
 - A 1 is stored in the “cell”
 - If the NMOS is present the word line activates the NMOS:
 - The word line is pulled-down by the NMOS
 - A 0 is stored in the cell

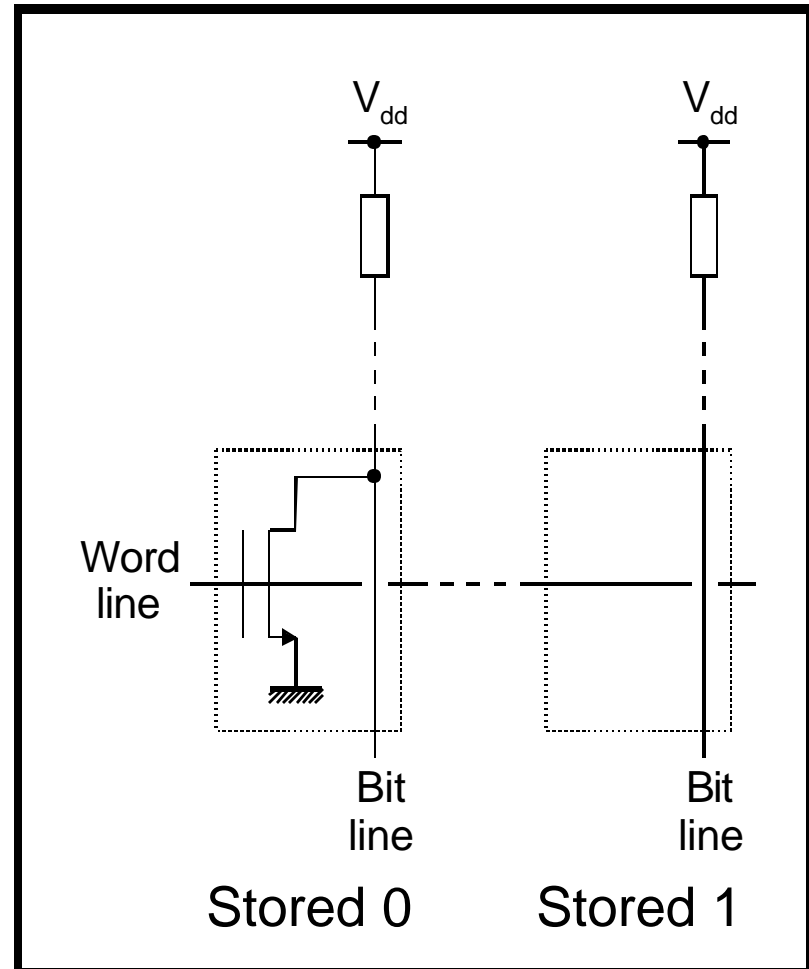

Read-only

 - In practice a “always on” pull-up device is never used because:
 - V_{OL} would depend on the ratio of the pull-up/pull-down devices
 - A static current path would exist when the output is low causing high power dissipation in large memories
- In practice pre-charged logic is used:
 - Eliminates the static dissipation
 - Pull-up devices can be made wider




- The bit lines are first pre-charged by the pull-up devices
 - during this phase the word lines must be disabled
- Then, the word lines are activated (word evaluation)
 - during this phase the pull-up devices are off

Nonvolatile R/W

- The same architecture as a ROM memory
- The pull-down device is modified to allow control of the threshold voltage
- The modified threshold is retained “indefinitely”:
 - The memory is nonvolatile
- To reprogram the memory the programmed values must be erased first
- The “heart” of NVRW memories is the Floating Gate Transistor (FAMOS)


Nonvolatile R/W

 - A floating gate is inserted between the gate and the channel
- The device acts as a normal transistor
- However, its threshold voltage is programmable
- Since the t_{ox} is doubled, the transconductance is reduced to half and the threshold voltage increased




Nonvolatile R/W

- Programming the FAMOS:
 - A high voltage is applied between the source and the gate-drain
 - A high field is created that causes avalanche injection to occur
 - Electrons traverse the first oxide and get trapped on the floating gate ($t_{ox} = 100\text{nm}$)
 - Trapped electrons effectively drop the floating gate voltage
 - The process is self limiting: the building up of gate charge eventually stops avalanche injection
 - The FAMOS with a charged gate is equivalent to a higher V_T device
 - Normal circuit voltages can not turn a programmed device on

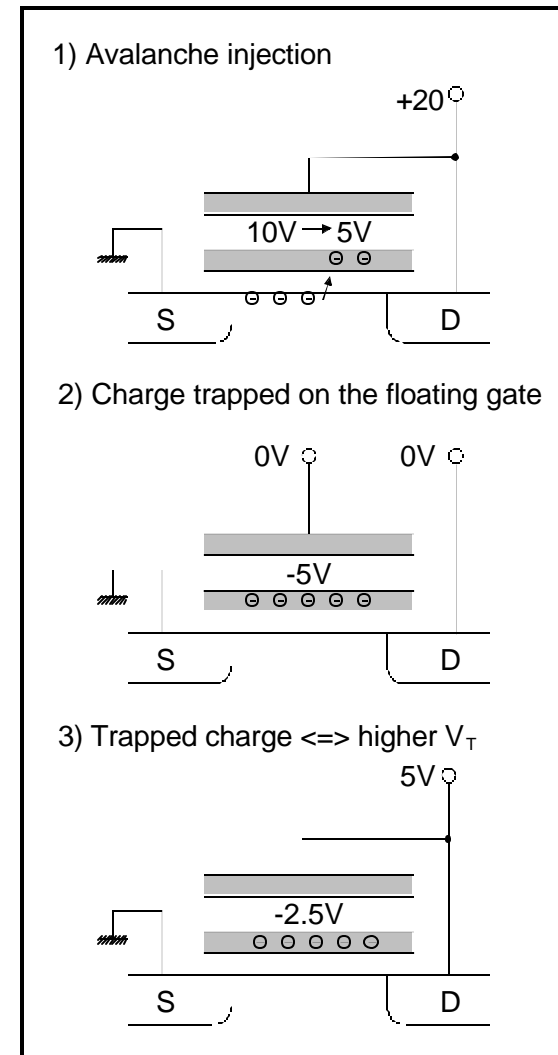

Nonvolatile R/W

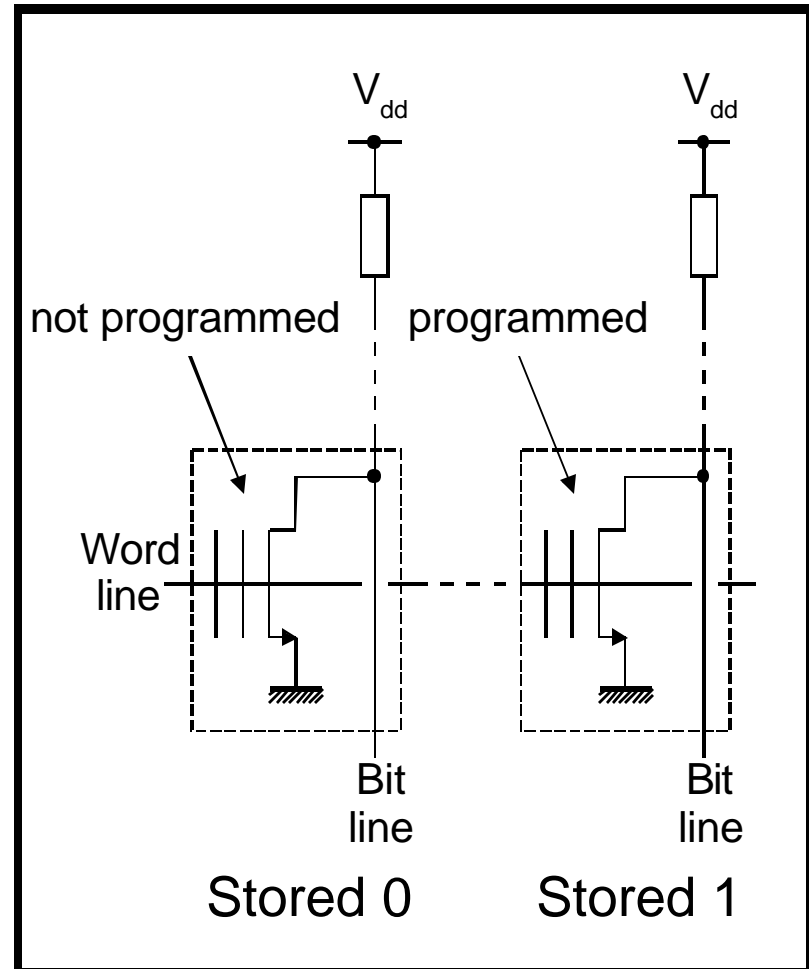- The non-programmed device can be turned on by the word line thus, it stores a “0”
- The word line high voltage can not turn on the programmed device thus, it stores a “1”
- Since the floating gate is surrounded by SiO_2 , the charge can be stored for many years




Nonvolatile R/W

- Erasing the memory contents (EPROM):
 - Strong UV light is used to erase the memory:
 - UV light renders the oxide slightly conductive by direct generation of electron-hole pairs in the SiO_2
 - The erasure process is slow (several minutes)
 - Programming takes 5-10 μs /word
 - Number of erase/program cycles limited (<1000)
- Electrically-Erasable PROM (E²PROM)
 - A reversible tunneling mechanism allows E²PROM's to be both electrically programmed and erased


6T SRAM

- Static Read-Write Memories (SRAM):
 - data is stored by positive feedback
 - the memory is volatile
- The cell uses six transistors
- Read/write access is enabled by the word-line
- Two bit lines are used to improve the noise margin during the read/write operation
- During read the bit-lines are pre-charged to $V_{dd}/2$:
 - to speedup the read operation
 - to avoid erroneous toggling of the cell

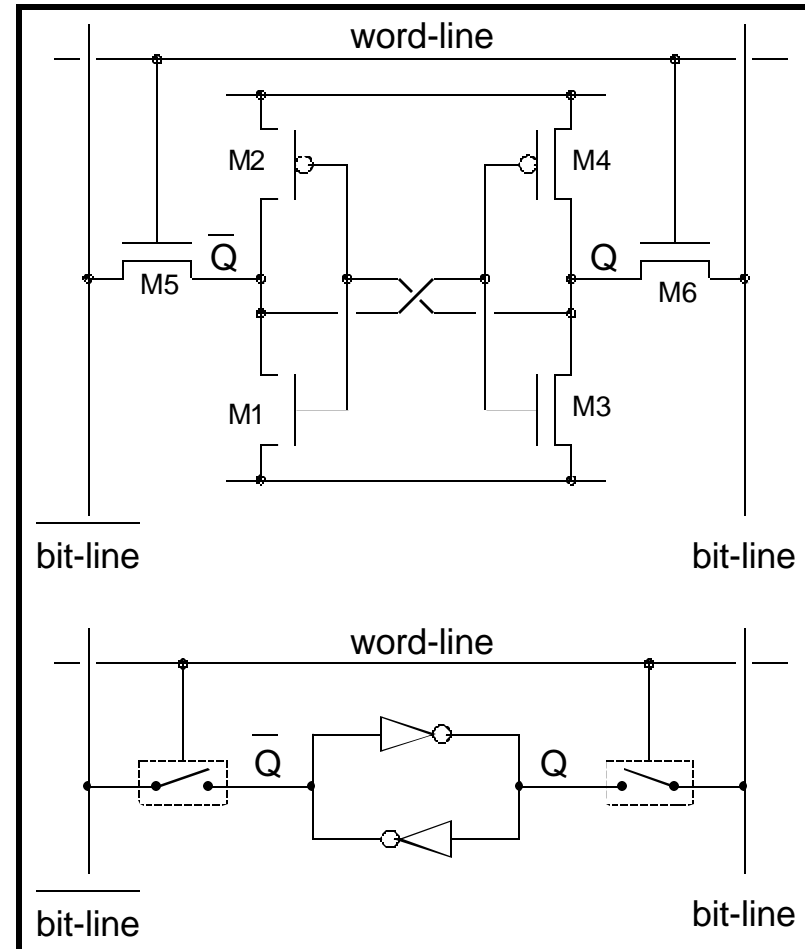


Resistive-load SRAM

- Resistive-load SRAM
 - employs resistors instead of PMOS's
 - The role of the resistors is only to maintain the state of the cell:
 - they compensate for leakage currents ($10^{-15}A$)
 - they must be made as high as possible to minimize static power dissipation
 - undoped polysilicon $10^{12}\Omega/\text{③}$
 - The bit-lines are pre-charged to V_{dd} :
 - the low-to-high transition occurs during precharge
 - the loads contribute “no” current during the transitions
 - The transistor sizes must be correctly chosen to avoid toggling the cell during read

 


3T Dynamic

- Dynamic Random-Access Memory (DRAM)
 - In a dynamic memory the data is stored as charge in a capacitor
- Tree-Transistor Cell (3T DRAM):
 - Write operation:
 - Set the data value in bit-line 1
 - Assert the write word-line
 - Once the WWL is lowered the data is stored as charge in C
 - Read operation:
 - The bit-line BL2 is pre-charged to V_{dd}
 - Assert the read word-line
 - if a 1 is stored in C, M2 and M3 pull the bit-line 2 low
 - if a 0 is stored C, the bit-line 2 is left unchanged

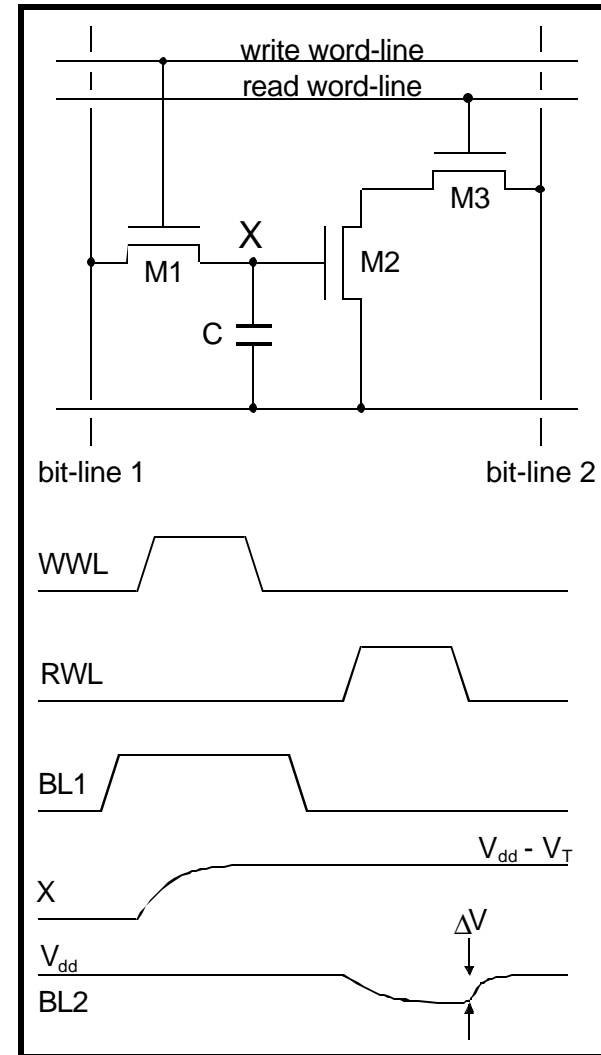

3T Dynamic


- The cell is inverting
- Due to leakage currents the cell needs to be periodically refreshed (every 1 to 4ms)
- Refresh operation:
 - read the stored data
 - put its complement in BL1
 - enable/disable the WWL
- Compared with an SRAM the area is greatly reduced:
 - SRAM $\Rightarrow 1092 \lambda^2$
 - DRAM $\Rightarrow 576 \lambda^2$
 - The area reduction is mainly due to the reduction of the number of devices and interlayer contacts

 

(from J. M. Rabaey 1996)

1T Dynamic

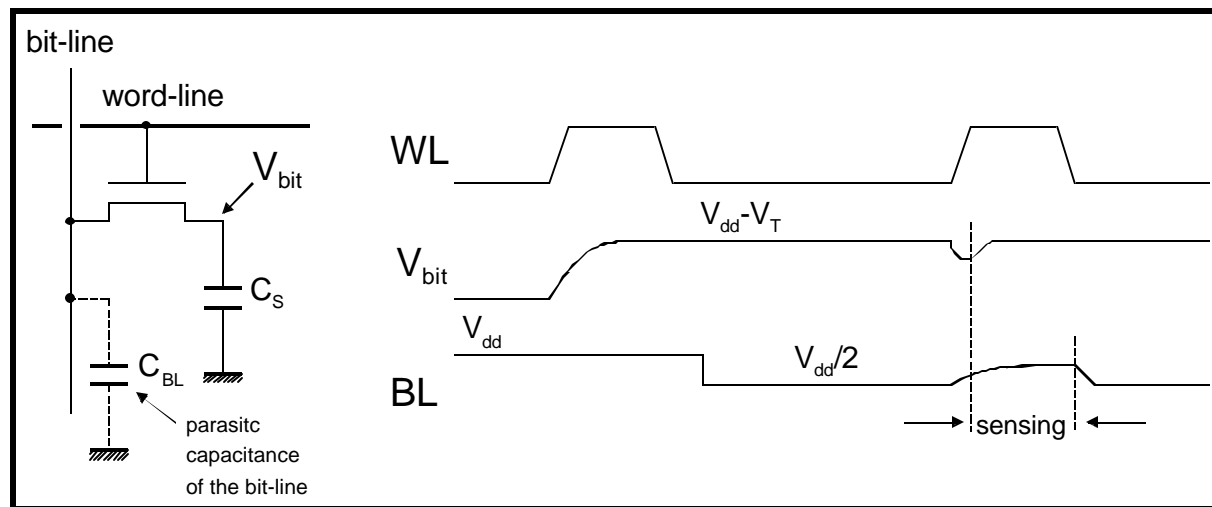- One-Transistor dynamic cell (1T DRAM)
 - It uses a single transistor and a capacitor
 - It is the most widely used topology in commercial DRAM's
- Write operation:
 - Data is placed on the bit-line
 - The word-line is asserted
 - Depending on the data value the capacitance is charged or discharged




1T Dynamic

- Read operation:
 - The bit-line is pre-charged to $V_{dd}/2$
 - The word-line is activated and charge redistribution takes place between C_S and the bit-line
 - This gives origin to a voltage change in the bit-line, the sign of which determines the data stored:

$$\Delta V = \left(V_{BIT} - \frac{V_{dd}}{2} \right) \frac{C_S}{C_S + C_{BL}}$$

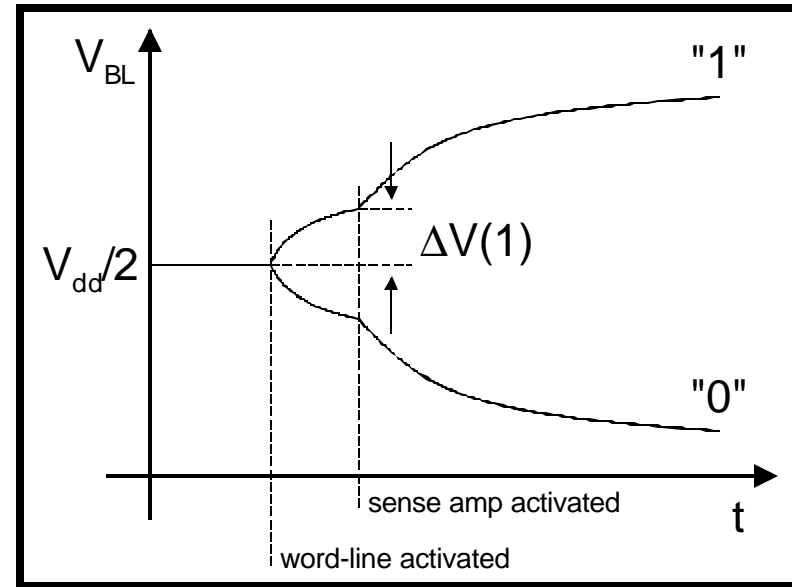
- C_{BL} is 10 to 100 times bigger than $C_S \Rightarrow \Delta V \approx 250\text{mV}$



- The amount of charge stored in the cell is modified during the read operation
- However, during read, the output of the sense amplifier is imposed on the bit line restoring the stored charge

1T Dynamic

 - Contrary to the previous cases a 1T cell requires a sense amplifier for correct operation
- Also, a relatively large storage capacitance is necessary for reliable operation
- A 1 is stored as $V_{dd} - V_T$. This reduces the available charge:
 - To avoid this problem the word-line can be bootstrapped to a value higher than V_{dd}



(from T. Mano et al., 1987)


Outline

- Introduction – *“Is there a limit?”*
- Transistors – *“CMOS building blocks”*
- Parasitics – *“The [un]desirables”*
- The CMOS inverter – *“A masterpiece”*
- Gates – *“Just like LEGO”*
- Sequential circuits – *“Time also counts!”*
- Storage elements – *“A bit in memory”*
- **Technology scaling – *“..., faster!”***
- Technology – *“Building an inverter”*

Technology scaling

- Scaling objectives
- Scaling variables
- Scaling consequences:
 - Device area
 - Transistor density
 - Gate capacitance
 - Drain current
 - Gate delay
 - Power
 - Power density
 - Interconnects

Scaling, why is it done?

 

Technology scaling

- Technology scaling has a threefold objective:
 - Increase the transistor density
 - Reduce the gate delay
 - Reduce the power consumption
- At present, between two technology generations, the objectives are:
 - Doubling of the transistor density;
 - Reduction of the gate delay by 30% (43% increase in frequency);
 - Reduction of the power by 50% (at 43% increase in frequency);

Technology scaling

- How is scaling achieved?
 - All the device dimensions (lateral and vertical) are reduced by $1/\alpha$
 - Concentration densities are increased by α
 - Device voltages reduced by $1/\alpha$ (not in all scaling methods)
 - Typically $1/\alpha = 0.7$ (30% reduction in the dimensions)

Technology scaling

- The **scaling variables** are:

- Supply voltage: $V_{dd} \rightarrow V_{dd} / \alpha$
- Gate length: $L \rightarrow L / \alpha$
- Gate width: $W \rightarrow W / \alpha$
- Gate-oxide thickness: $t_{ox} \rightarrow t_{ox} / \alpha$
- Junction depth: $X_j \rightarrow X_j / \alpha$
- Substrate doping: $N_A \rightarrow N_A \times \alpha$

This is called **constant field** scaling because the electric field across the gate-oxide does not change when the technology is scaled

If the power supply voltage is maintained constant the scaling is called **constant voltage**. In this case, the electric field across the gate-oxide increases as the technology is scaled down.

Due to gate-oxide breakdown, below 0.8 μ m only “constant field” scaling is used.

Scaling consequences

Some consequences of 30% scaling in the constant field regime ($\alpha = 1.43$, $1/\alpha = 0.7$):

- Device/die area:

$$W \times L \rightarrow (1/\alpha)^2 = 0.49$$

- In practice, microprocessor die size grows about 25% per technology generation! This is a result of added functionality.

- Transistor density:

$$(\text{unit area}) / (W \times L) \rightarrow \alpha^2 = 2.04$$

- In practice, memory density has been scaling as expected. (not true for microprocessors...)

Scaling consequences

- Gate capacitance:

$$W \times L / t_{ox} \rightarrow 1/\alpha = 0.7$$

- Drain current:

$$(W/L) \times (V^2/t_{ox}) \rightarrow 1/\alpha = 0.7$$

- Gate delay:

$$(C \times V) / I \rightarrow 1/\alpha = 0.7$$

$$\text{Frequency} \rightarrow \alpha = 1.43$$

- In practice, microprocessor frequency has doubled every technology generation (2 to 3 years)! This faster increase rate is due to highly pipelined architectures (“less gates per clock cycle”)

Scaling consequences

- Power:

$$C \times V^2 \times f \rightarrow (1/\alpha)^2 = 0.49$$

- In reality power consumption increases due to added functionality.

- Power density:

$$1/t_{\text{ox}} \times V^2 \times f \rightarrow 1$$

- Active capacitance/unit-area:

Power dissipation is a function of the operation frequency, the power supply voltage and of the circuit size (number of devices).

If we normalize the power density to $V^2 \times f$ we obtain the active capacitance per unit area for a given circuit. This parameter can be compared with the oxide capacitance per unit area:

$$1/t_{\text{ox}} \rightarrow \alpha = 1.43$$

- In practice, for microprocessors, the active capacitance/unit-area only increases between 30% and 35%. Thus, the twofold improvement in logic density between technologies is not achieved.

Scaling consequences

- Interconnects scaling:
 - Higher densities are only possible if the interconnects also scale.
 - Reduced width → increased resistance
 - Denser interconnects → higher capacitance
 - To account for increased parasitics and integration complexity **more interconnection layers** are added:
 - thinner and tighter layers → local interconnections
 - thicker and sparser layers → global interconnections and power

Interconnects are scaling as expected

Scaling consequences

Parameter	Constant Field	Constant Voltage	
Supply voltage (V_{dd})	$1/\alpha$	1	<p>Scaling Variables</p>
Length (L)	$1/\alpha$	$1/\alpha$	
Width (W)	$1/\alpha$	$1/\alpha$	
Gate-oxide thickness (t_{ox})	$1/\alpha$	$1/\alpha$	
Junction depth (X_j)	$1/\alpha$	$1/\alpha$	
Substrate doping (N_A)	α	α	
Electric field across gate oxide (E)	1	α	<p>Device Repercussion</p>
Depletion layer thickness	$1/\alpha$	$1/\alpha$	
Gate area (Die area)	$1/\alpha^2$	$1/\alpha^2$	
Gate capacitance (load) (C)	$1/\alpha$	$1/\alpha$	
Drain-current (I_{dss})	$1/\alpha$	α	
Transconductance (g_m)	1	α	
Gate delay	$1/\alpha$	$1/\alpha^2$	<p>Circuit Repercussion</p>
Current density	α	α^3	
DC & Dynamic power dissipation	$1/\alpha^2$	α	
Power density	1	α^3	
Power-Delay product	$1/\alpha^3$	$1/\alpha$	