

ANALOGUE CIRCUITS

TECHNIQUES

Part II

April 16th , 2002
F. ANGHINOLFI
CERN

Francis.Anghinolfi@cern.ch

Outline

From “active” components available in modern IC technologies, to the examples of amplifiers design used for High Energy Physics applications


- 1- Introduction to analogue circuit
- 2- Active elements in Integrated Circuit
- 3- The bipolar transistor

Outline

- 4- Basic of amplifier
 - 5- Differential amplifier
 - 6- OTA
 - 7- Two-stage differential amplifier
 - 8- Other amplifiers circuits
 - 9- Cascode circuits
-
- 10- Charge Sensitive Preamplifier
 - 11- Transimpedance Preamplifier
 - 12- Preamplifiers conclusions

10 – Charge Sensitive Preamplifier

Reminder :

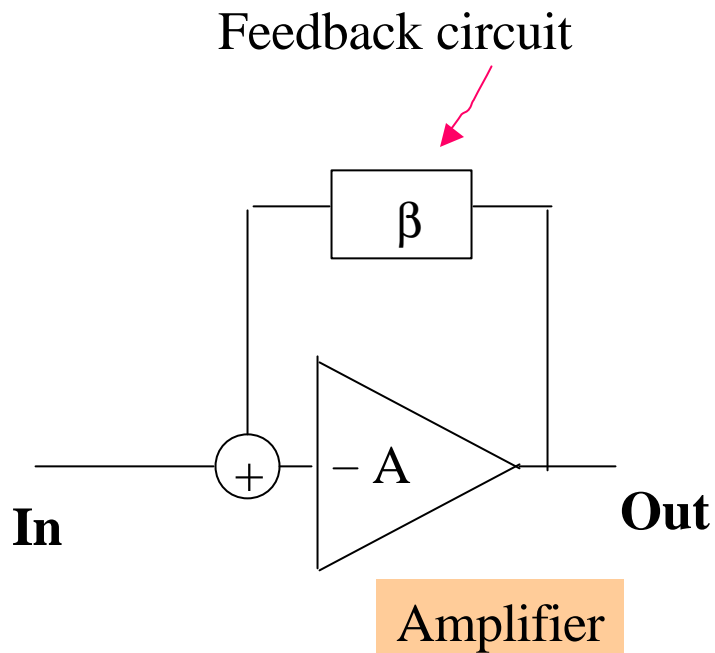

A = Forward Path gain

β = Feedback gain


$A \beta$ = Open Loop Gain

$$\text{Out/In} = \frac{A}{1 + A\beta} = \text{Closed Loop Gain}$$

Stability is assumed if the Open Loop Gain ($A \beta$, complex number) is far away from -1

10 – Charge Sensitive Preamplifier

Reminder :

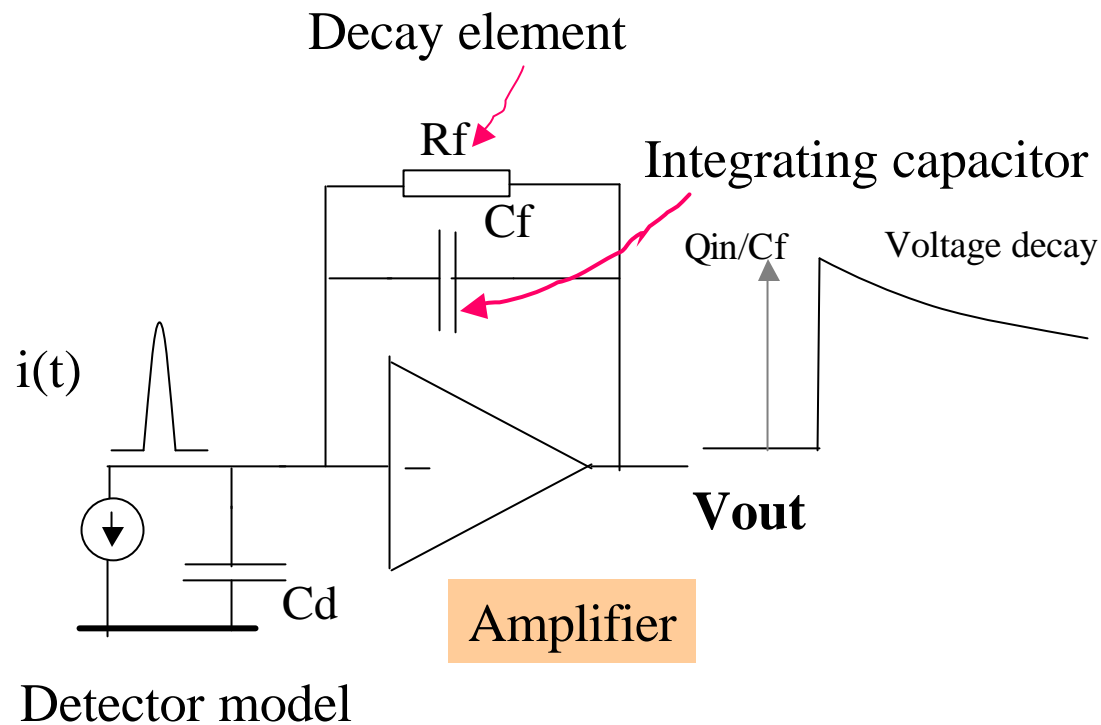


$$Q_{in} = \int_0^t i(t) dt$$

The charge is integrated on the feedback capacitance (C_f)

$$V_{out} = \frac{Q_{in}}{C_f}$$

The output voltage V_{out} decays with $R_f \cdot C_f$ time constant (pile-up problem)

10 – Charge Sensitive Preamplifier

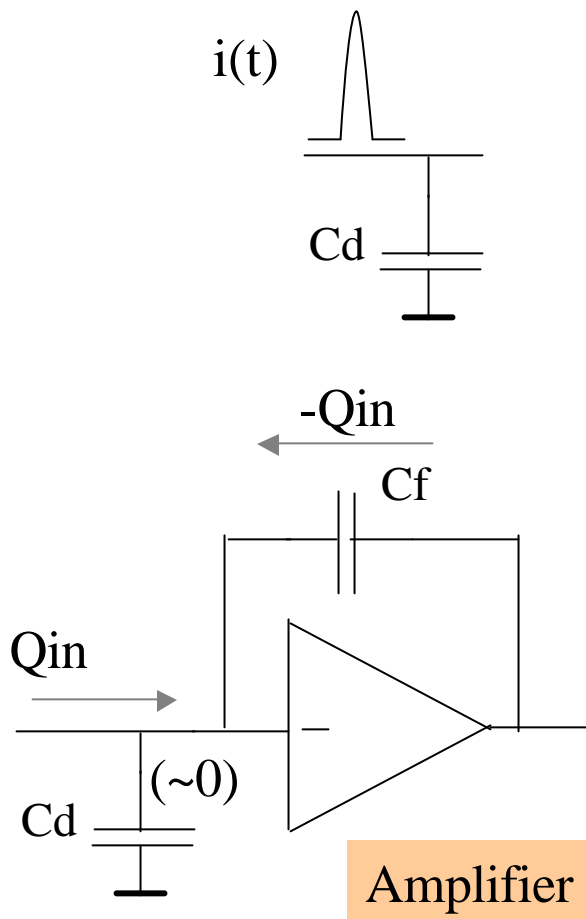

Charge from detector builds up a voltage on the detector node capacitance

$$V_{det} = \frac{Q_{in}}{C_d}$$


The preamplifier reacts in such a way that its input node voltage stays unchanged : the output voltage V_{out} is moving to the point where :

$$V_{out} \cdot C_f = -Q_{in}$$

The input node charge (also voltage) variation is zero

10 – Charge Sensitive Preamplifier

Frequency domain

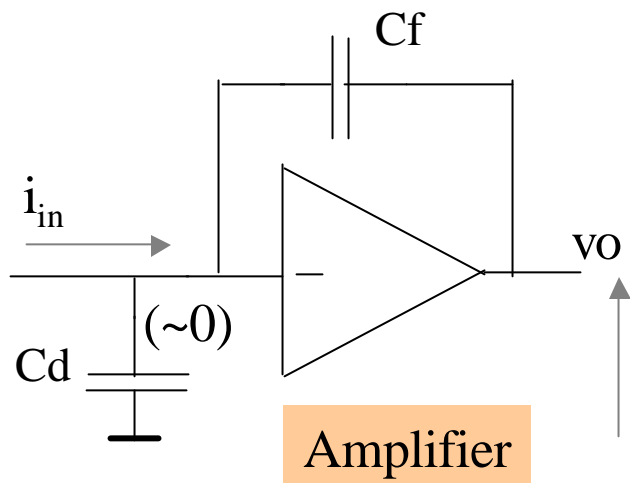


In case of an ideal amplifier (infinite gain, no BW limit) :

$$V_O = \frac{i_{in}}{s \cdot C_f}$$

10 – Charge Sensitive Preamplifier



Frequency domain

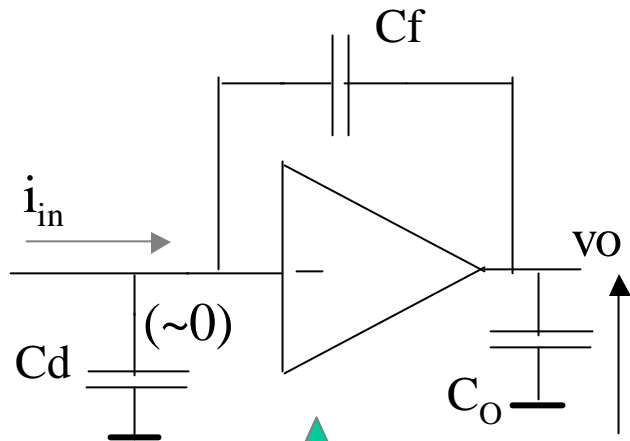

Consider now a non-ideal amplifier, loaded with capacitance C_o :

$$\frac{v_o}{v_{in}} = \frac{g_m \cdot R_L}{1 + sC_o \cdot R_L}$$

Amplifier

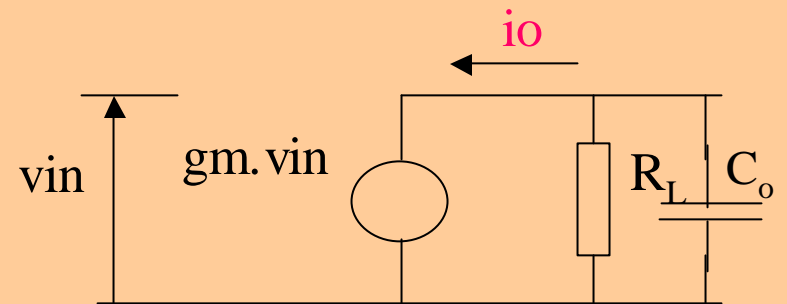
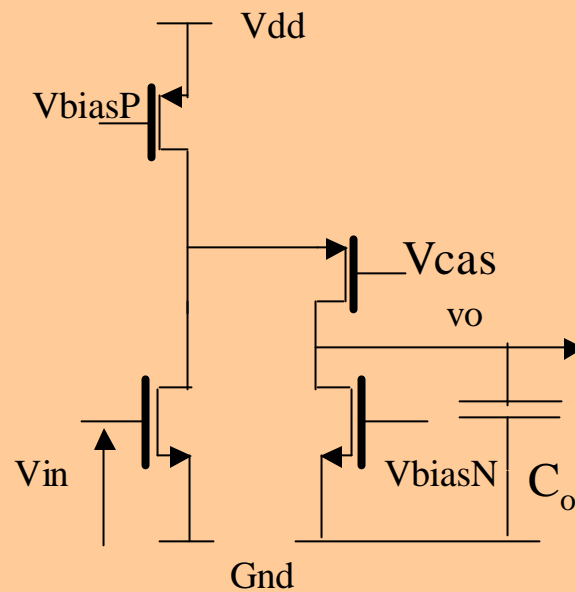


Small signal model

10 – Charge Sensitive Preamplifier

Frequency domain

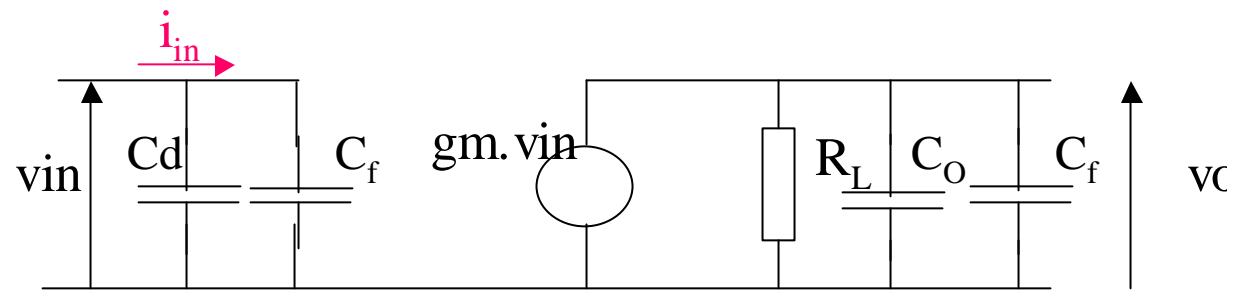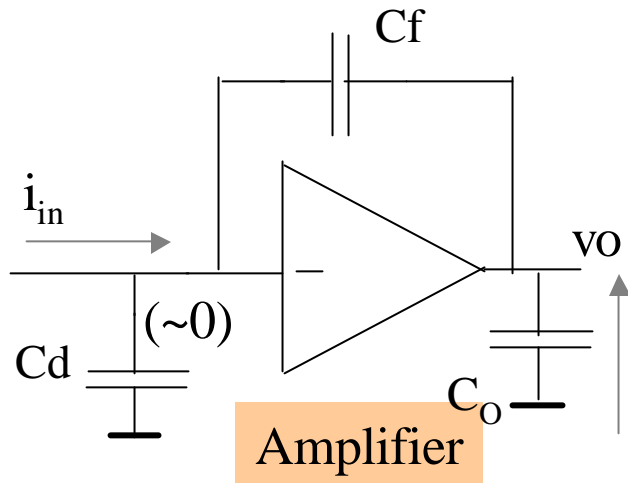If we consider C_f acting not as a feedback element, but just as a capacitive load on input and output (forward path gain A) :





Small signal model

$$\frac{v_{in}}{i_{in}} = \frac{1}{s(C_d + C_f)}$$

$$\frac{v_o}{v_{in}} = \frac{g_m \cdot R_L}{1 + s(C_o + C_f) \cdot R_L}$$

10 – Charge Sensitive Preamplifier

Frequency domain

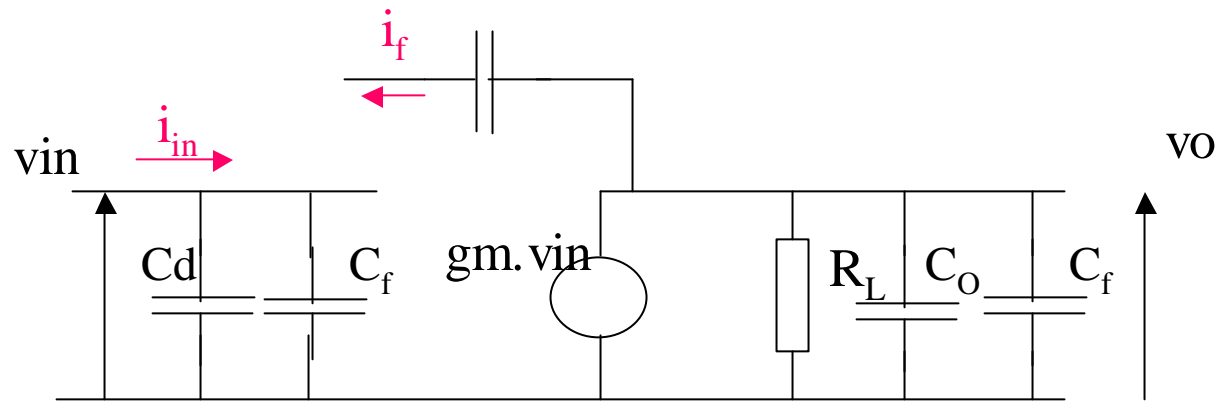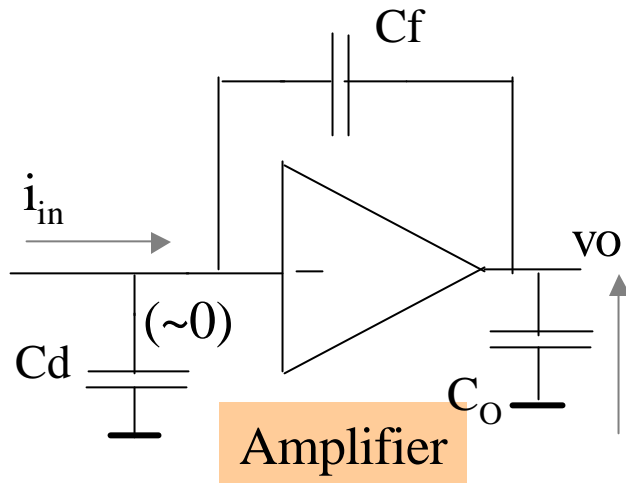

Forward Gain
(A)


$$\frac{V_O}{i_{in}} = \frac{gm \cdot R_L}{1 + s(C_o + C_f) \cdot R_L} \cdot \frac{1}{s(C_d + C_f)}$$

Feedback Gain
(β)

$$\frac{i_f}{V_O} = s \cdot C_f$$

10 – Charge Sensitive Preamplifier

Frequency domain

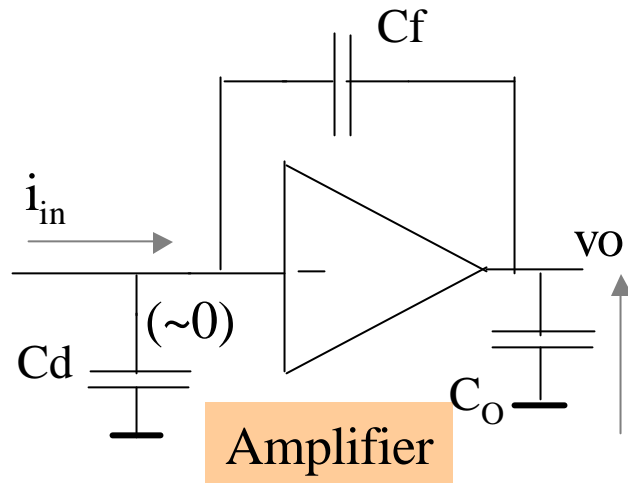

Open loop Gain formula

$$\frac{i_f}{i_{in}} = A.\beta$$

In our case, the product $A\beta$ is :


$$A\beta = \frac{gm.R_L}{1 + s(Co + Cf).R_L} \cdot \frac{Cf}{(Cd + Cf)}$$

$A\beta$ is a one pole system, such that $1+A\beta$ cannot be zero.

The charge preamplifier is difficult to make unstable

10 – Charge Sensitive Preamplifier

Frequency domain

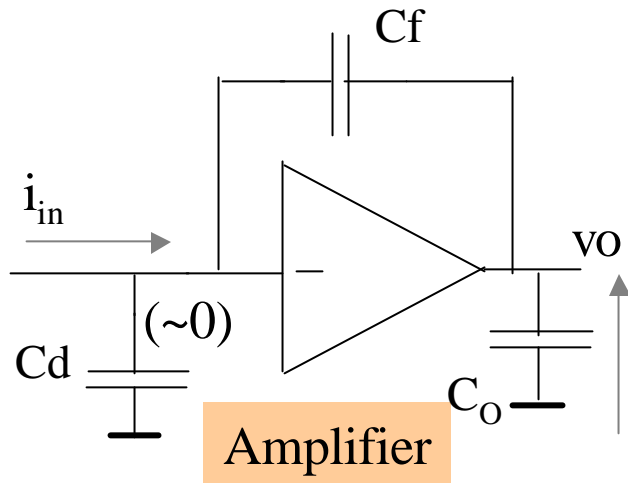

Closed loop Gain Calculation

$$\frac{v_o}{i_{in}} = \frac{A}{1 + A\beta}$$

$$\frac{v_o}{i_{in}} = \frac{1}{sC_f} \cdot \frac{1}{1 + s \frac{(C_d + C_f)(C_o + C_f)}{g_m \cdot C_f}}$$

Ideal Integrator response



Pole added by amplifier limited BW

10 – Charge Sensitive Preamplifier

Frequency domain

It can be shown that the input impedance of the charge preamplifier is given by :
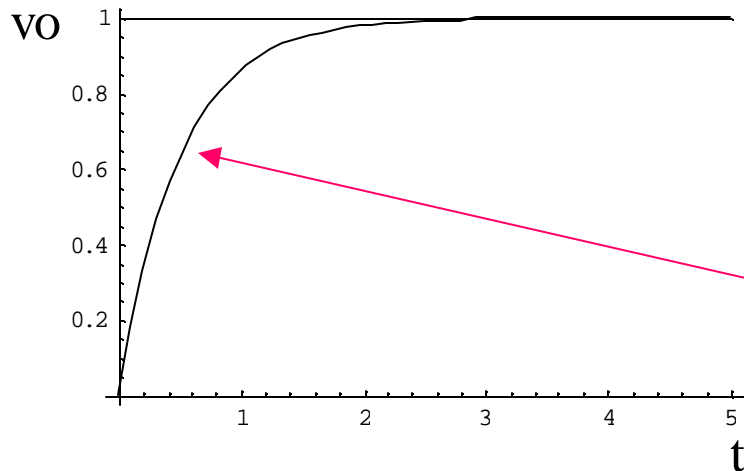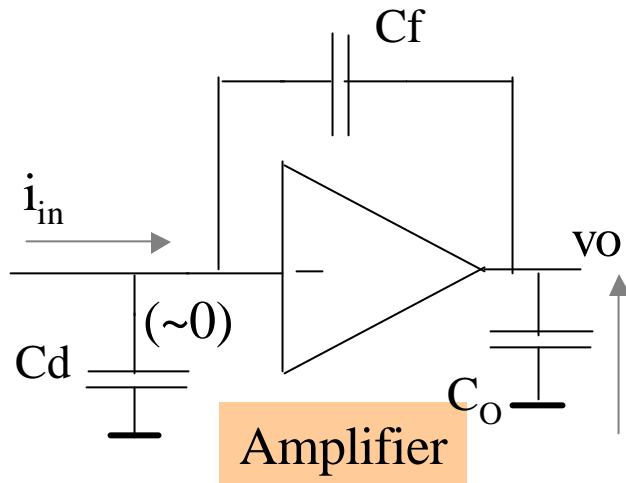
$$R_{in} = \frac{(C_o + C_f)}{g_m \cdot C_f}$$



$$\frac{v_o}{i_{in}} = \frac{1}{sC_f} \cdot \frac{1}{1 + sR_{in} \cdot (C_d + C_f)}$$

Input node RC time constant



10 – Charge Sensitive Preamplifier

Frequency domain

Numerical values

$C_f=0.1\text{pF}$, $R_o = 500\text{K}$, $C_o=1\text{pF}$, $C_{in}=20\text{pF}$

$g_m=0.003\text{S}$

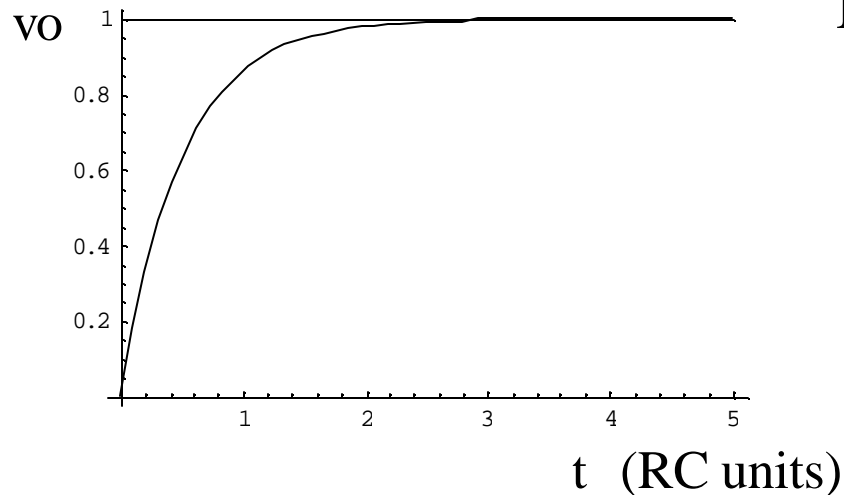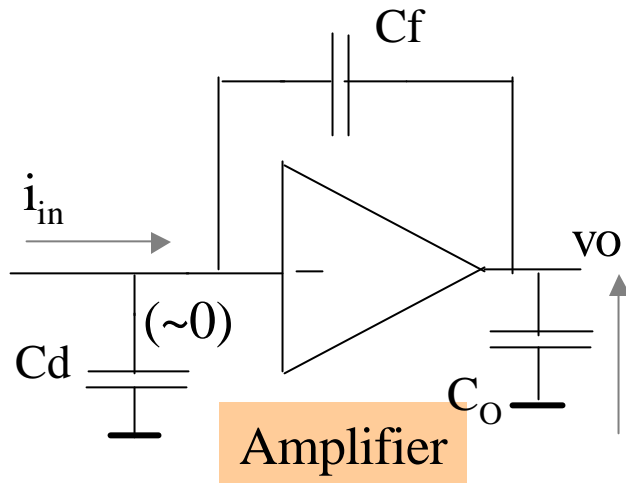


$$R_{in} = \frac{(C_o + C_f)}{g_m \cdot C_f} \quad \text{gives} \quad R_{in} = 3.7 \text{ Kohms}$$

$$\frac{v_o}{i_{in}} = \frac{1}{sC_f} \cdot \frac{1}{1 + sR_{in} \cdot (C_d + C_f)}$$

Input node RC time constant=75ns

10 – Charge Sensitive Preamplifier

With Resistive feedback element

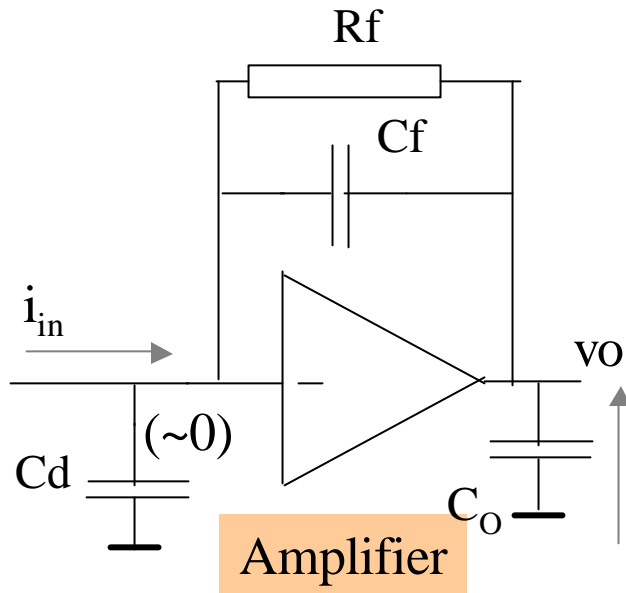


$$\frac{v_o}{i_{in}} = \frac{1}{sC_f} \cdot \frac{R_f}{1 + s \cdot R_f \cdot C_f} \cdot \frac{1}{1 + sR_{in} \cdot (C_d + C_f)}$$


Feedback RC

Input node RC


RfCf=500RinCin

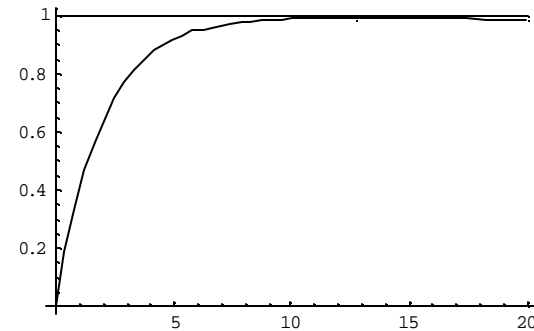

RfCf=50RinCin

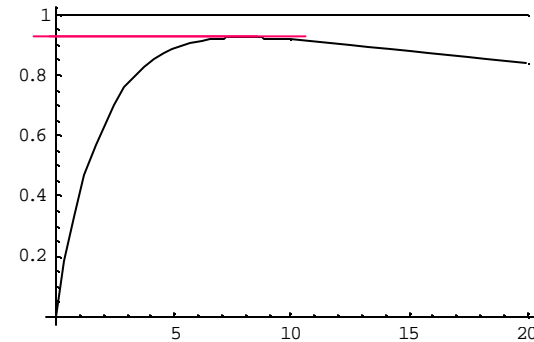


RfCf=5RinCin

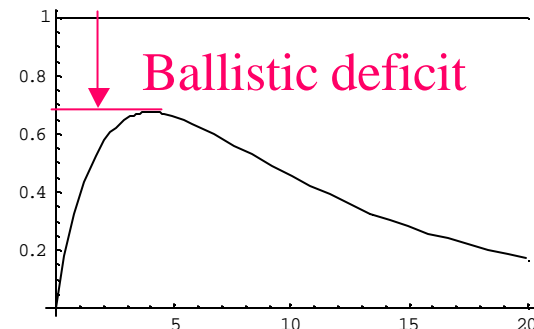

10 – Charge Sensitive Preamplifier

Charge collection time

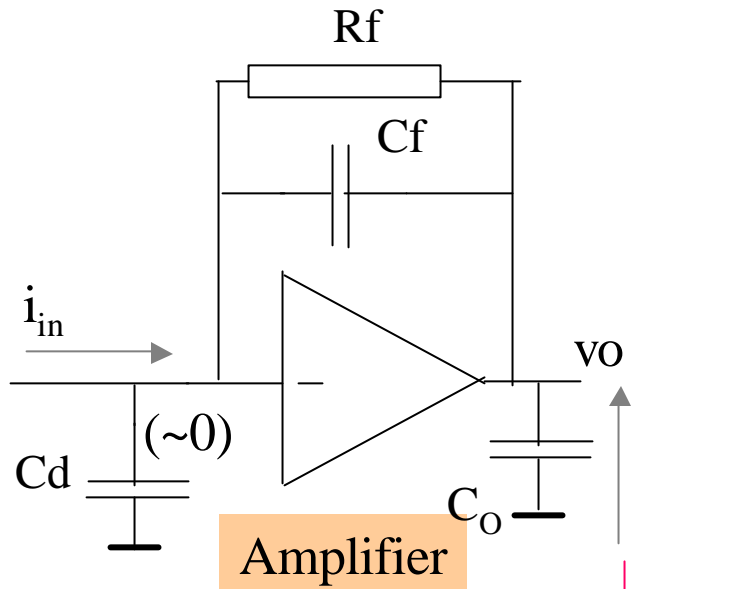



$$\frac{v_o}{i_{in}} = \frac{1}{sC_f} \cdot \frac{R_f}{1 + s \cdot R_f \cdot C_f} \cdot \frac{1}{1 + sR_{in} \cdot (C_d + C_f)}$$

Feedback RC


Input node RC

$R_f C_f = 50 R_{in} C_{in}$

Instant charge

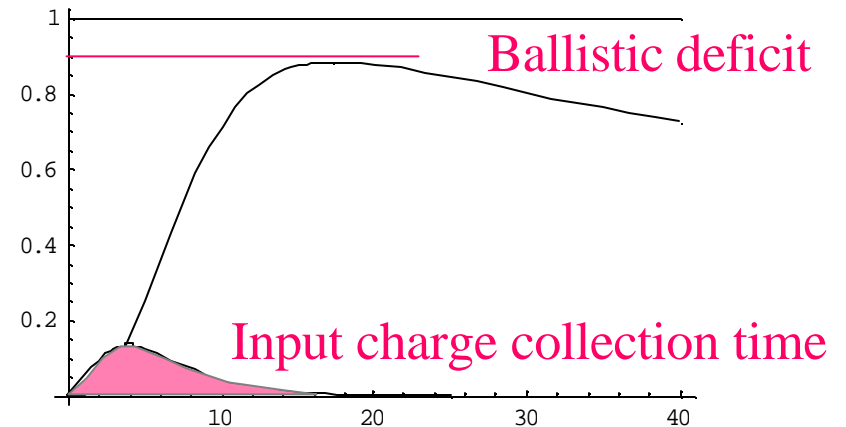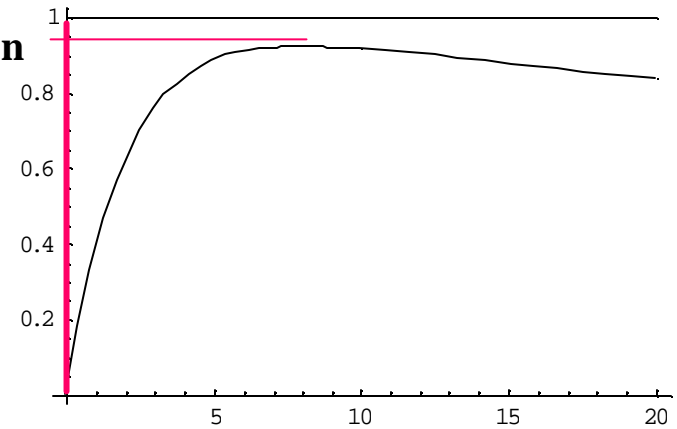

11 – Transimpedance Preamplifier

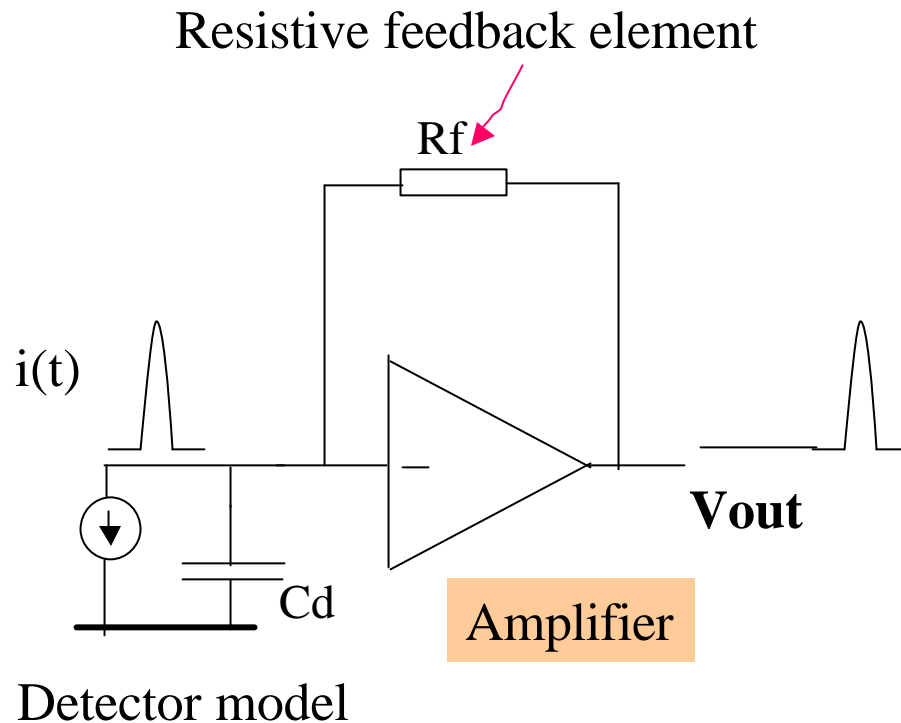


$$(Q_{in} = \int_0^t i(t) dt)$$

$$V_{out}(t) = R_f \cdot i_{in}(t)$$


The instantaneous output voltage is the image of the current flow at the detector output (ideal case !)

11 – Transimpedance Preamplifier

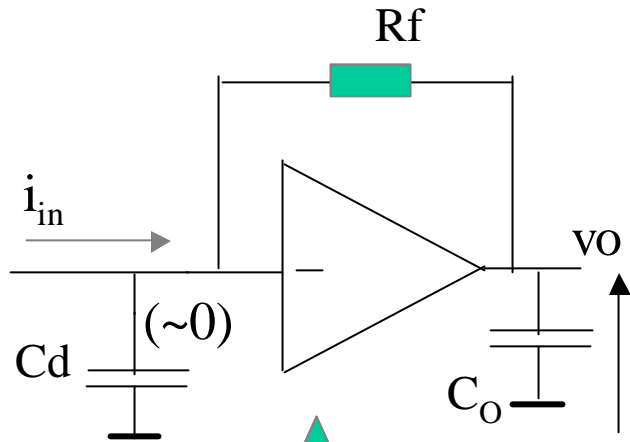

Frequency domain

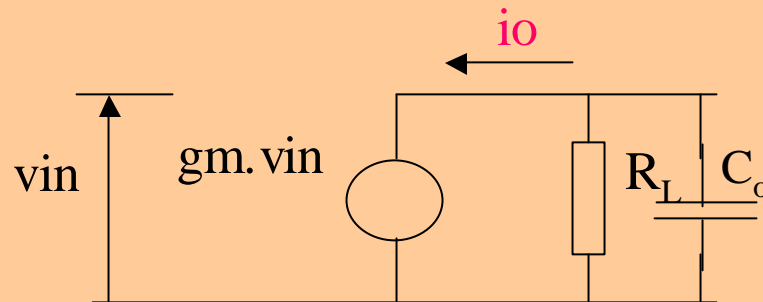Consider now a non-ideal amplifier, loaded with capacitance C_o :



Small signal model



$$\frac{v_o}{v_{in}} = \frac{g_m \cdot R_L}{1 + sC_o \cdot R_L}$$

Amplifier

11 – Transimpedance Preamplifier

Frequency domain

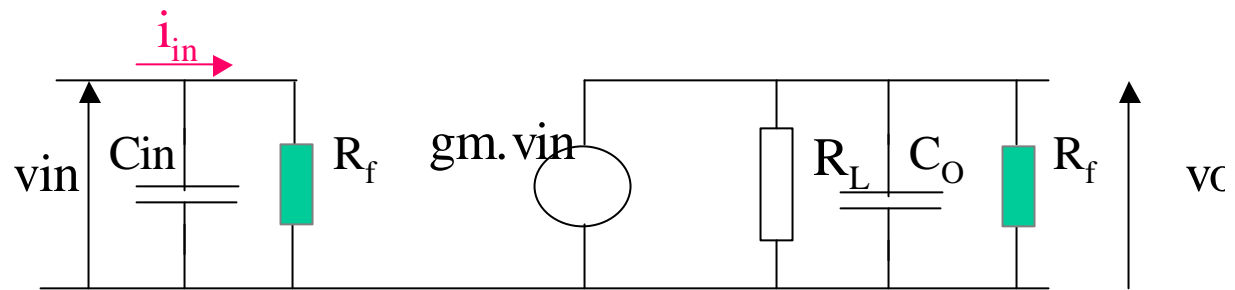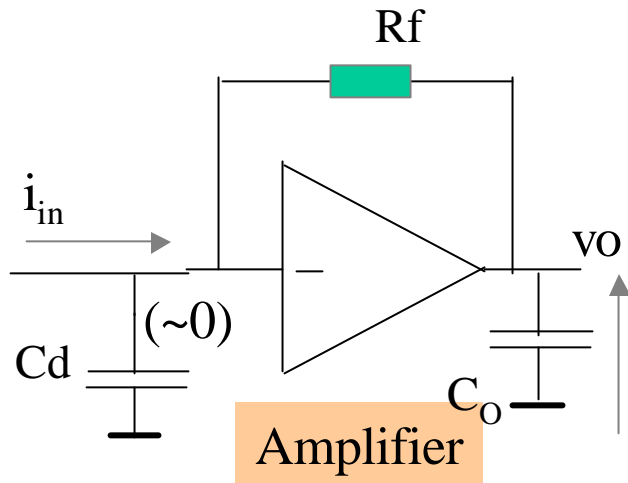If we consider R_f acting not as a feedback element, but just as a resistive load on input and output (forward path gain A) :



Small signal model



$$\frac{v_{in}}{i_{in}} = \frac{R_f}{1 + s.R_f.C_{in}}$$

$$\frac{v_o}{v_{in}} = \frac{g_m.R_o}{1 + s.R_o.C_o}$$

With $R_o = R_f // R_L$

11 – Transimpedance Preamplifier

Frequency domain

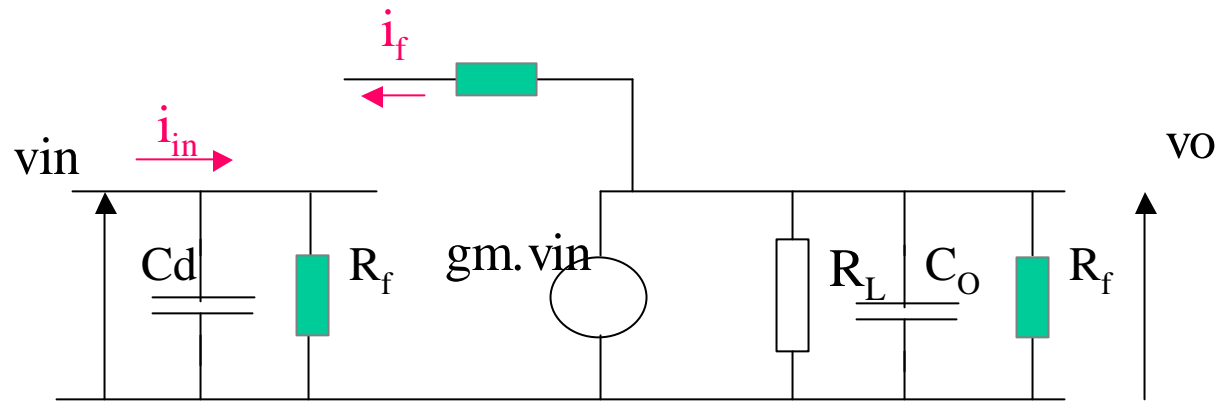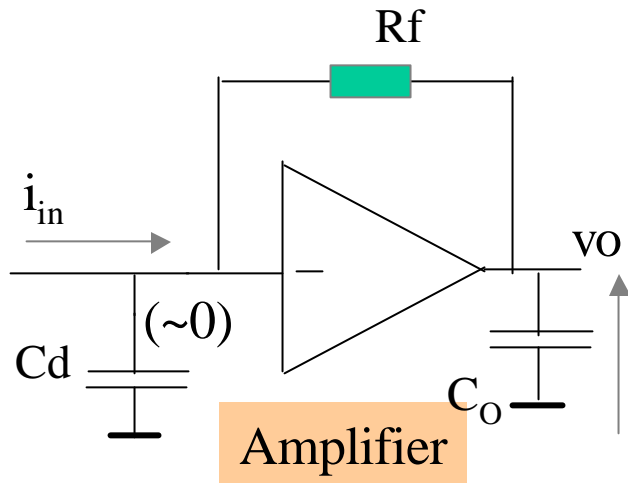


Forward Gain (A)
$$\frac{v_o}{i_{in}} = \frac{g_m \cdot R_o}{1 + s \cdot C_o \cdot R_o} \cdot \frac{R_f}{1 + s \cdot R_f \cdot C_{in}} \quad (R_o = R_f // R_L)$$

Feedback Gain (β)
$$\frac{i_f}{v_o} = \frac{1}{R_f}$$

11 – Transimpedance Preamplifier

Frequency domain

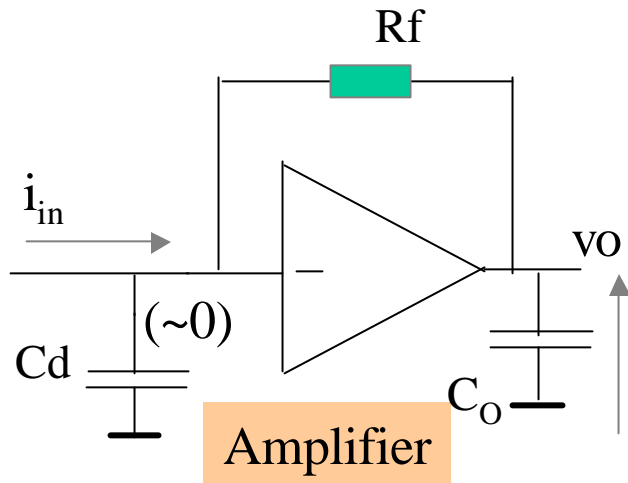

Open loop Gain formula

$$\frac{i_f}{i_{in}} = A.\beta$$

The open loop gain (product $A\beta$) is :


$$A\beta = \frac{gm.Ro}{(1 + s.Co.Ro)(1 + s.Cin.Rf)} \quad (Ro=R_f//R_L)$$

$A\beta$ has two poles, $1+A\beta$ can be zero, and the closed loop circuit being unstable

The transimpedance preamplifier is difficult to make stable

11 – Transimpedance Preamplifier

Frequency domain

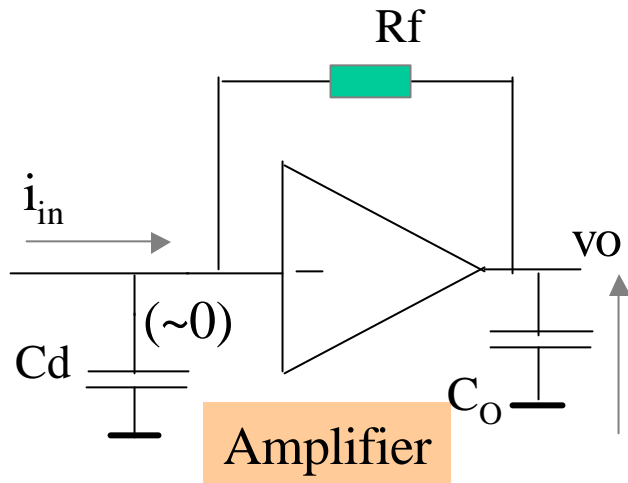

Closed loop Gain Calculation

$$\frac{v_O}{i_{in}} = \frac{A}{1 + A\beta}$$


$$\frac{v_O}{i_{in}} = R_f \cdot \frac{1}{1 + \frac{(1 + s.R_o.C_o)(1 + s.C_{in}.R_f)}{A_0}}$$

Ideal transimpedance response

Two poles circuit response

$$(R_o = R_f // R_L) \text{ and } A_0 = g_m.R_o$$

11 – Transimpedance Preamplifier

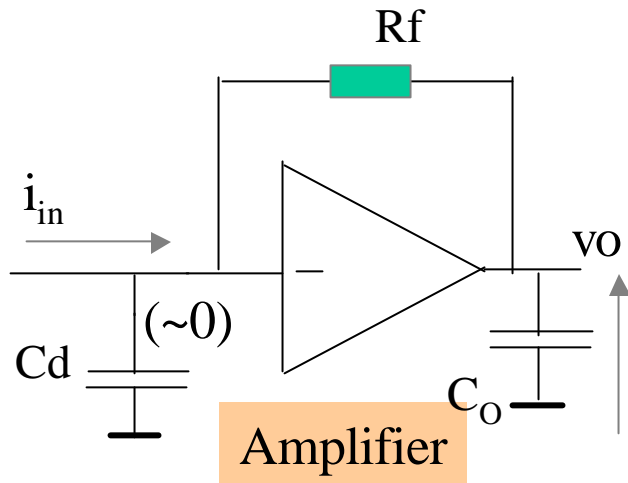

Under the strong assumption that poles $C_{in}/R_f.A_0$ and $R_o.C_o$ are widely separated :

$$\frac{v_O}{i_{in}} \approx R_f \cdot \frac{1}{\left(1 + s \cdot \frac{C_{in} \cdot R_f}{A_0}\right) (1 + s \cdot R_o \cdot C_o)}$$

It can be shown that the input impedance of the transimpedance preamplifier is given by :


$$R_{in} = \frac{R_f}{A_0}$$

$$\frac{v_O}{i_{in}} \approx R_f \cdot \frac{1}{(1 + s R_{in} \cdot C_{in}) (1 + s R_o \cdot C_o)}$$

Two real pole circuit

11 – Transimpedance Preamplifier

Widely spaced poles

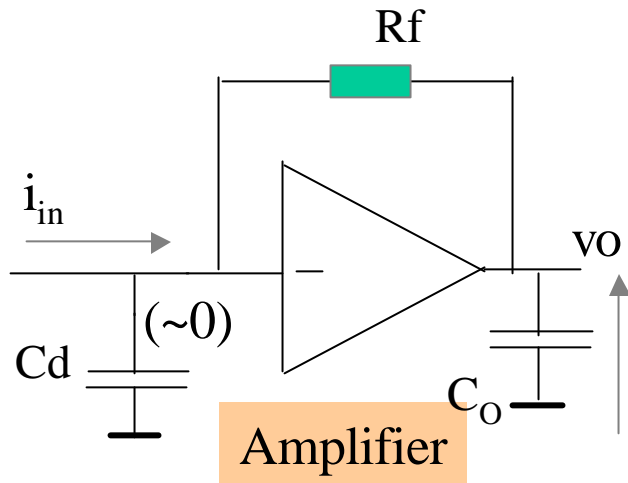


Numerical values :

$R_f=30K$, $R_o = 500K$, $C_o=0.1pF$, $C_{in}=200pF$

$g_m=0.001S$
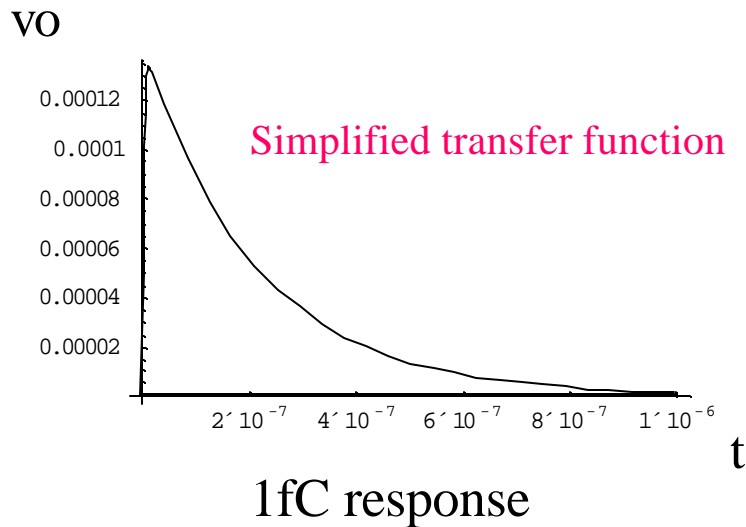
$$R_{in} = \frac{R_f}{A_0} \quad \text{gives} \quad R_{in} = 1Kohms$$




$$\frac{v_O}{i_{in}} \approx R_f \cdot \frac{1}{(1 + sR_{in}.C_{in})(1 + sR_o.C_o)}$$

Input node RC time constant
 $R_{in}.C_{in}= 200ns$

Internal pole
 $R_o.C_o= 3ns$

11 – Transimpedance Preamplifier

Widely spaced poles

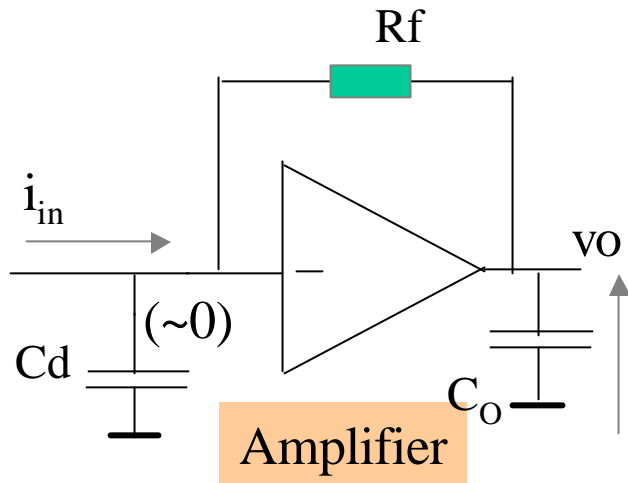


Numerical values :

$R_f=30K$, $R_o = 500K$, $C_o=0.1pF$, $C_{in}=200pF$

$g_m=0.001S$


Computing the true transfer function with the same numerical values :
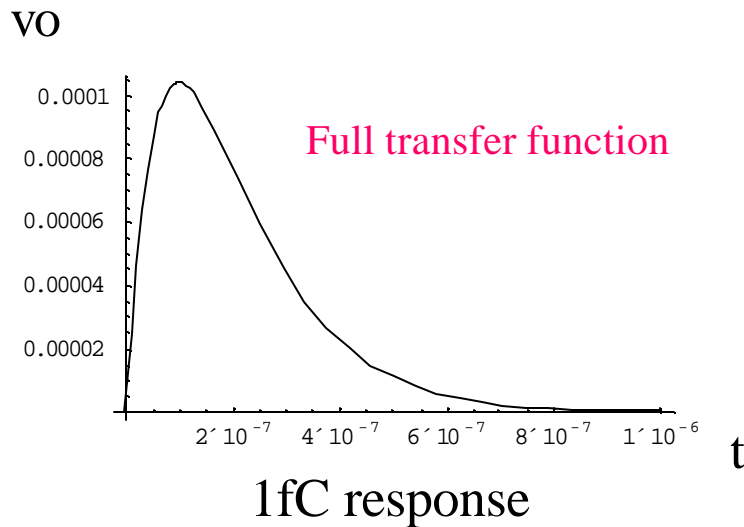
$$\frac{v_o}{i_{in}} = R_f \cdot \frac{1}{1 + \frac{(1 + s \cdot R_o \cdot C_o)(1 + s \cdot C_{in} \cdot R_f)}{A_0}}$$



11 – Transimpedance Preamplifier

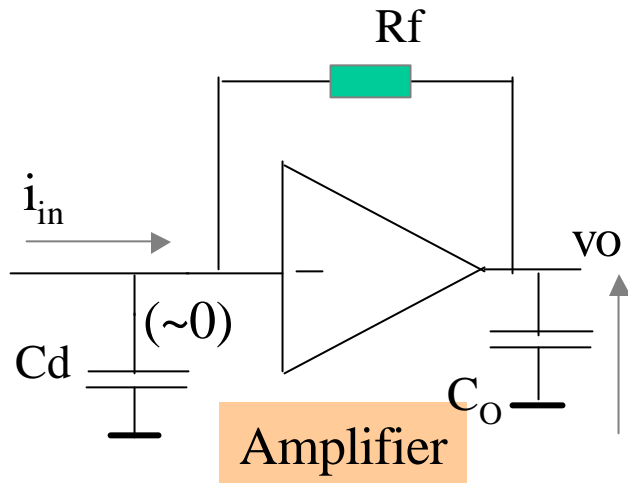Example with some realistic numbers, fast preamplifier



Consider numerical values fitting with silicon strip detector :

$R_f=30K$, $R_o = 500K$, $C_o=0.1pF$, $C_{in}=20pF$


$g_m=0.003S$

Computing the true transfer function :

$$\frac{v_o}{i_{in}} = R_f \cdot \frac{1}{1 + \frac{(1 + s.R_o.C_o)(1 + s.C_{in}.R_f)}{A_0}}$$


The circuit is close to instability !

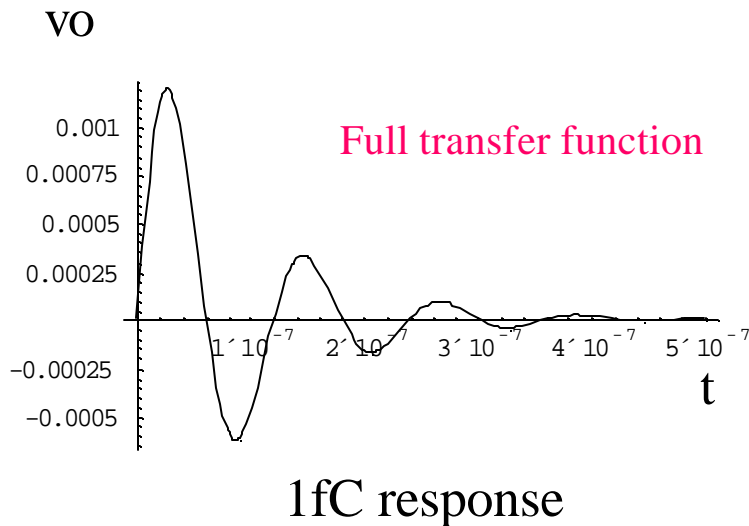(equivalent input impedance 300 ohms, $R_{in}C_{in}=7ns$, $R_oC_o=3ns$)



11 – Transimpedance Preamplifier

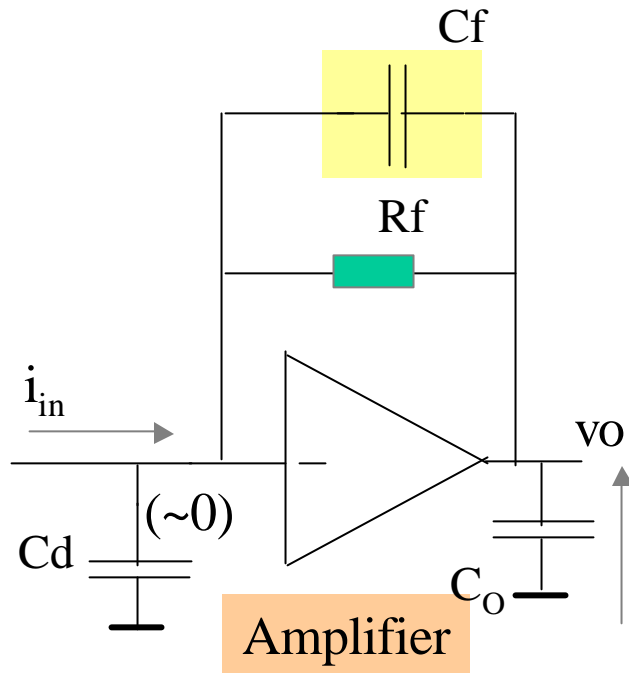Example with some realistic numbers, fast preamplifier



Transimpedance stability is obtained by the addition of the feedback capacitance C_f

The open loop gain (product $A\beta$) is changed as:

$$A\beta = \frac{A_o \cdot (1 + s \cdot C_f \cdot R_f)}{(1 + s \cdot C_o \cdot R_o)(1 + s \cdot C_{in} \cdot R_f)}$$

$$(R_o = R_f // R_L) \quad \text{and} \quad A_o = g_m \cdot R_o$$


If $C_f \cdot R_f$ is made equal to $C_o \cdot R_o$ time constant :

$$A\beta = \frac{A_o}{(1 + s \cdot C_{in} \cdot R_f)}$$

The circuit becomes stable

11 – Transimpedance Preamplifier

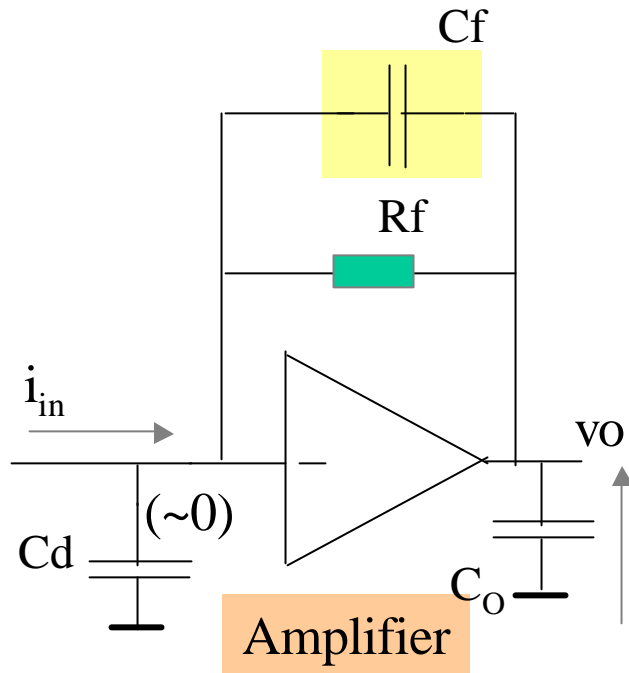Example with some realistic numbers, fast preamplifier



Transimpedance stability is obtained by the addition of the feedback capacitance Cf


Closed loop Gain Calculation

If Cf.Rf is made equal to Co.Ro time constant :

$$\frac{v_O}{i_{in}} = R_f \cdot \frac{1}{(1 + s \cdot R_o \cdot C_o) \left(1 + s \cdot \frac{C_{in} \cdot R_f}{A_o}\right)}$$

11 – Transimpedance Preamplifier

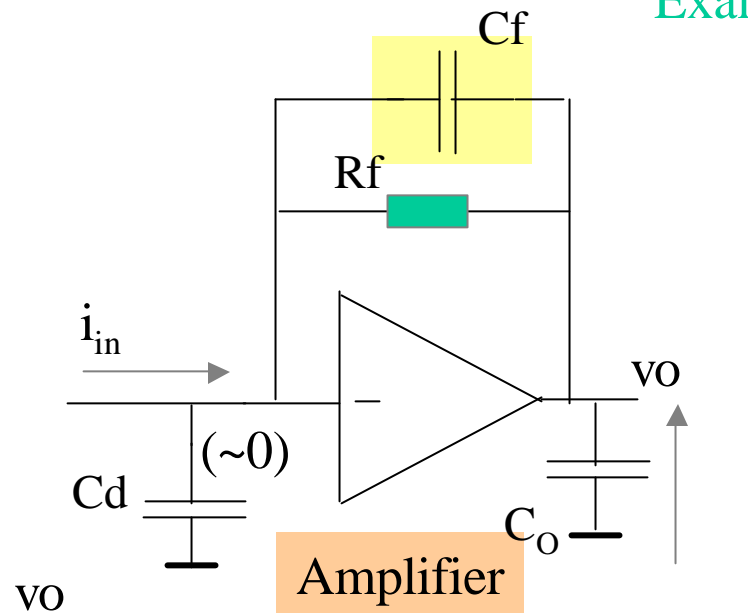Example with some realistic numbers, fast preamplifier



Numerical values :

$R_f=30K$, $R_o = 500K$, $C_o=0.1pF$, $C_{in}=20pF$

$g_m=0.003S$, $C_f=0.1pF$


$$R_{in} = \frac{R_f}{A_0} \quad \text{gives} \quad R_{in} = 350 \text{ohms}$$

$$\frac{v_o}{i_{in}} \approx R_f \cdot \frac{1}{\underbrace{\left(1 + s \cdot \frac{R_f}{A_0} \cdot C_{in}\right)}_{A_0} \cdot (1 + sR_o \cdot C_o)}$$

Input node RC time constant

$R_{in} \cdot C_{in} = 7 \text{ ns}$

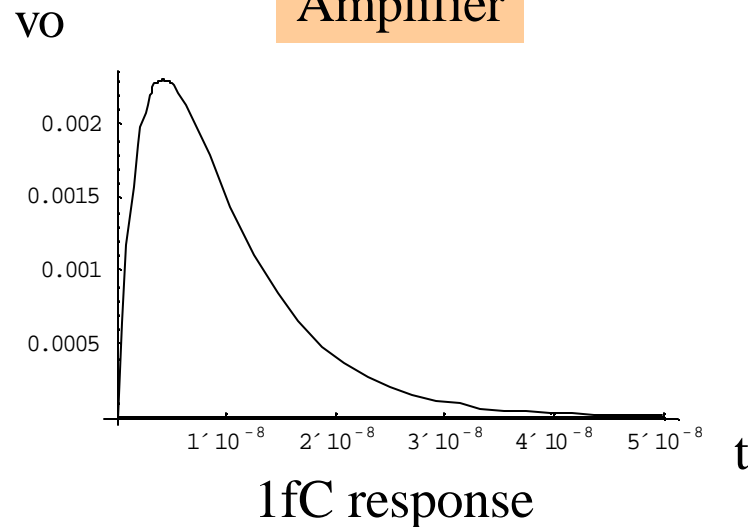Internal pole
 $R_o \cdot C_o = 3 \text{ ns}$



12 – Preamplifiers conclusions


	Charge Preamp	Transimpedance
Time constant	>50ns	>5ns
Input Impedance	Kohms range	100ohms range
Stability	Easy	Difficult
Gain	Q/Cf Ballistic deficit	Time response dependance

12 – Preamplifiers conclusions

Simplifications were done for all the preceding formulations:

We assumed main amplifiers with one pole only. In all cases, it is not true and amplifiers should be modeled with at least two internal poles

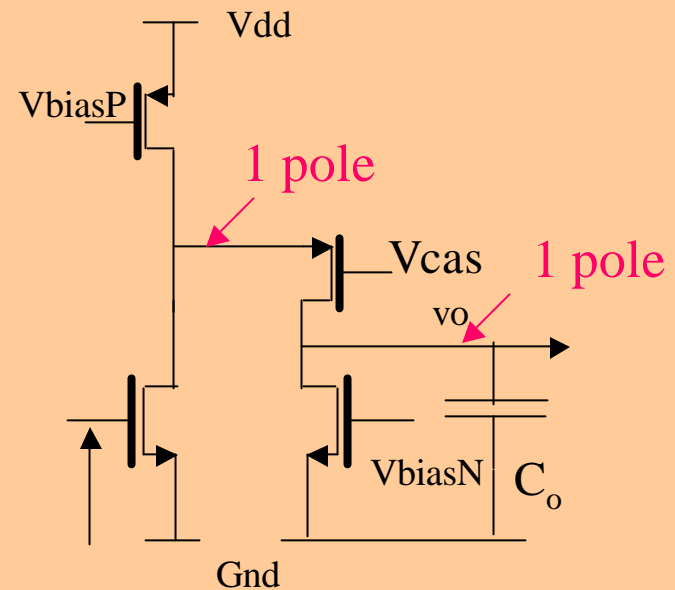The true closed loop gain formulations are in general complex. “Spice” simulations are mandatory to finalize the stability issue and predict precisely the transfer function



12 – Preamplifiers conclusions

During the preamplifier design discussions, we did not consider :

- The noise issue (sets constraints on gm, RC time constants)
- The signal gain and dynamic range

- Power supply noise rejection
- Common mode issue
-

V_{in}


A preamplifier design is a compromise between many aspects (specifications), the choice of a particular design will depend on :

- . The signal range and collection time
- . The S/N ratio (noise prediction)
- . The available power

Other parameters to consider :

- . Dynamic range & pile-up
- . Large signal recovery
- . PSRR, Common mode etc ...

12 – Preamplifiers conclusions

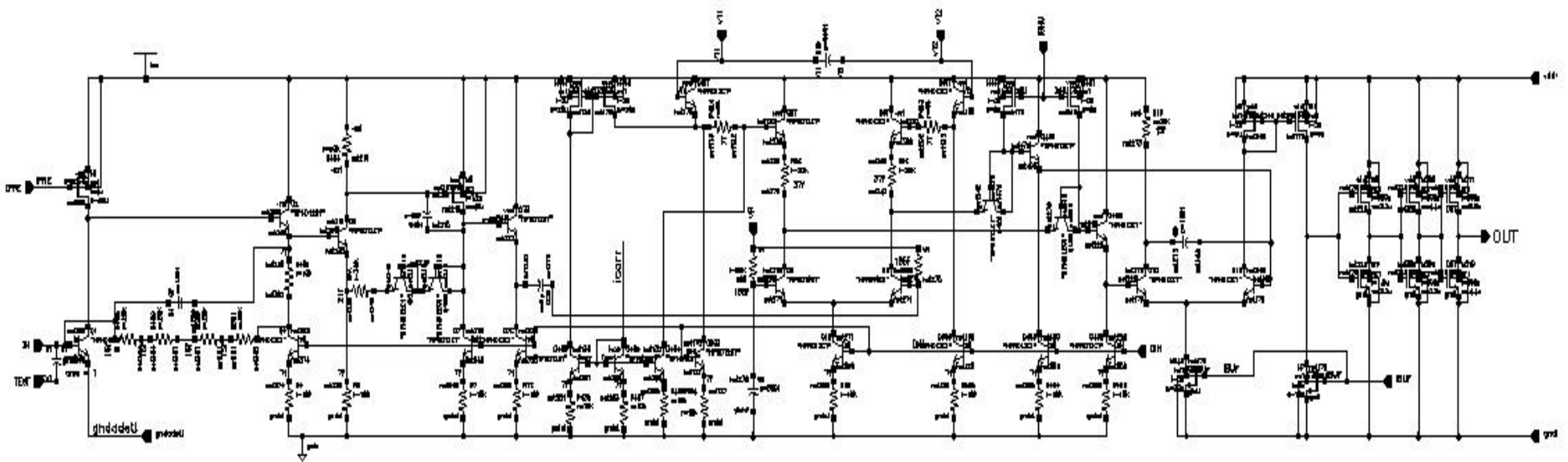

Low noise analog amplifier chain for Silicon Tracker BiCMOS 0.8 μ m, 20ns rise time

