



From Transistor Circuits (CMOS) to CHIP Case Study : Pipeline Analog to Digital Converter Design

Eri Prasetyo W.
Gunadarma University


Issues

- Software Tools Design
- CHIP Fabrication
- Cost
- How to design the transistor circuits into the CHIP




Software Tools Design

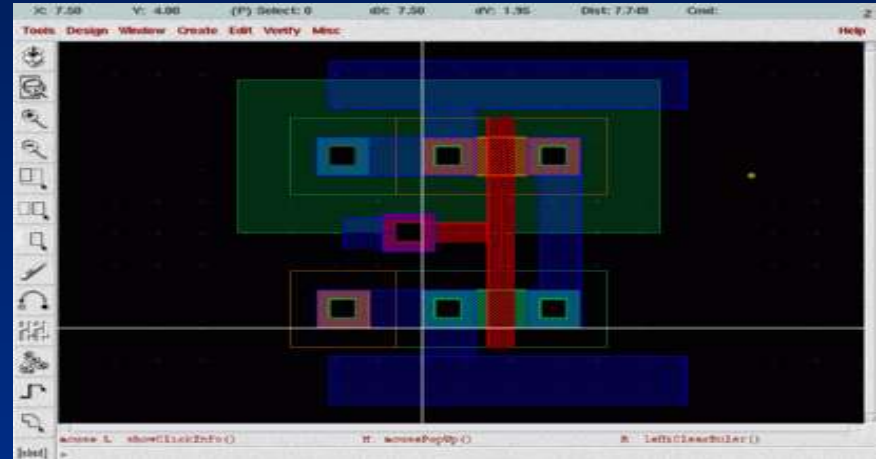- LASI,MAGIC,DREAI
- MAX,MyCAD LAYED
- Cadence




- Mentor Graphics
- Etc

 

CHIP Fabrication

 - CMP-TIMA, France
- TSMC, Taiwan
- NEC, Japan
- Mosis, USA
- Mimos, Malaysia ?
- Etc





Cost

- Austria Micro Systems
 - 0.6 CMOS CUP 390 Euro/mm²
 - 0.35 CMOS C35B4C3 650 Euro/mm²
- STMicroelectronics
 - 0.18 CMOS HCMOS8D 990 Euro/mm²
 - 0.12 CMOS HCMOS9GP 2500 Euro/mm²
 - 90 nm CMOS CMOS090 5000 Euro/mm²

How to design ...

Case : Pipeline ADC design

- First Step :
 - Architecture Circuit Design


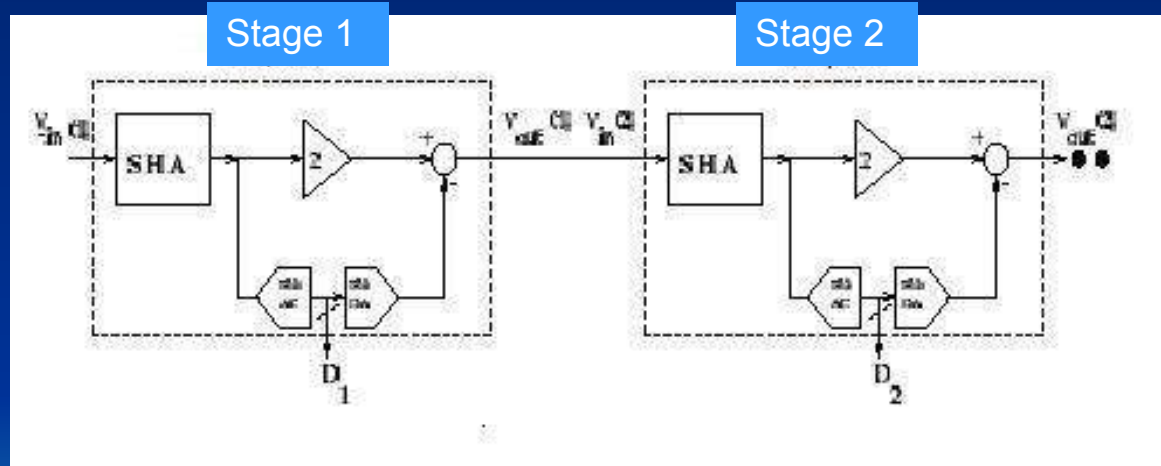


Diagram Block of One bit per stage


How to design ...

Case : Pipeline ADC design

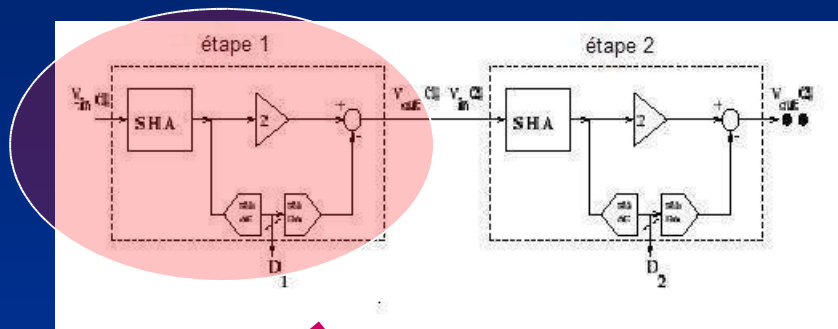- First Step :
 - Architecture Circuit Design



Implemented by
Switched Capacitor

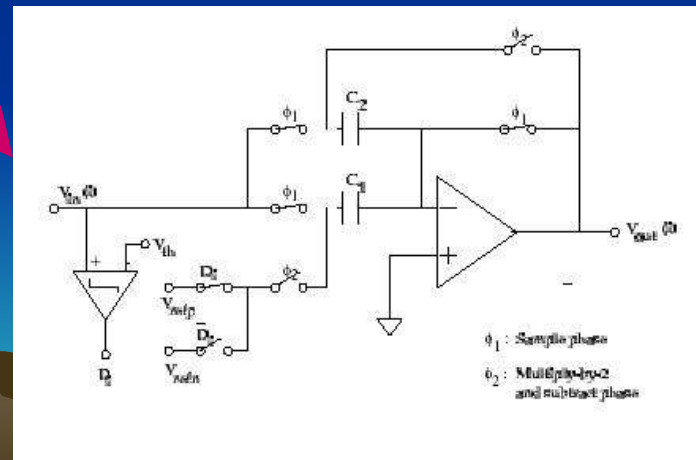


How to design ...

Case : Pipeline ADC design

- Each stage operates in two phase :
 - Sampling phase
 - Multiplying Phase


Sampling Phase

 

Sampling phase

1. V_{in} is stored in capacitors
2. Comparator produces a digital output D
 - ✓ $D = 1$ if $V_{in} > (V_{refp} - V_{refn}) / 2$
 - ✓ $D = 0$ if $V_{in} < (V_{refp} - V_{refn}) / 2$

Multiplying Phase

 

Multiplying phase

1. If $D = 1$
 - ✓ Capacitor $C1$ connect to V_{refp}
 - ✓ $V_{out} = 2 * V_{in} - V_{refp}$
2. If $D = 0$
 - ✓ Capacitor $C1$ connect to V_{refn}
 - ✓ $V_{out} = 2 * V_{in} - V_{refn}$

How to design ...



Case : Pipeline ADC design

- First Step :
 - Architecture Circuit Design

Comparator

Consists of three blocks :

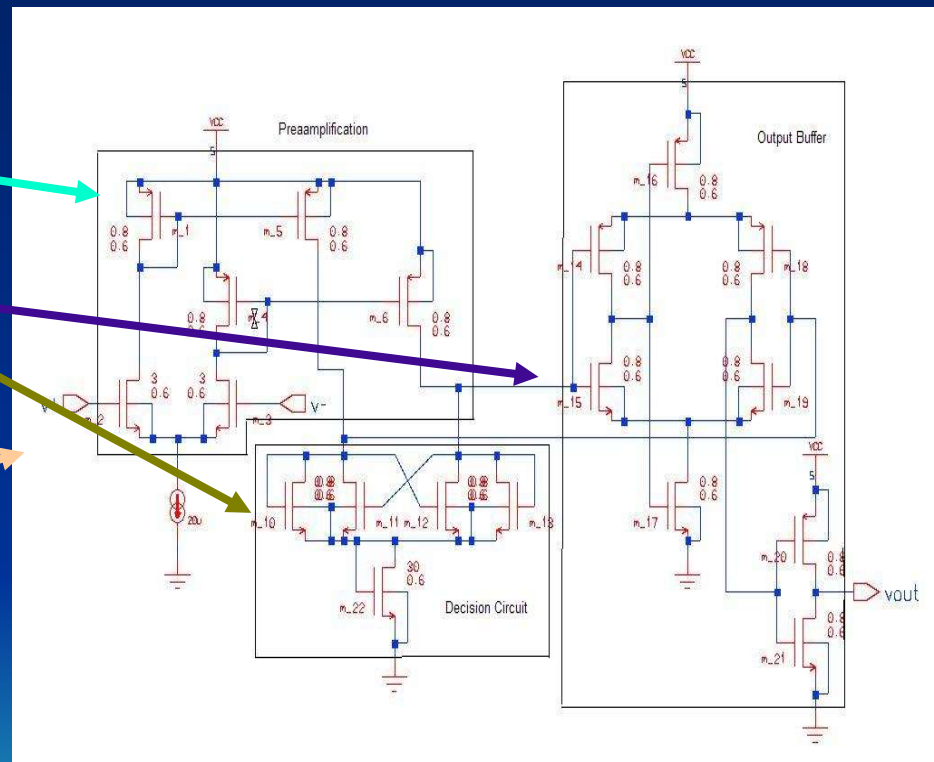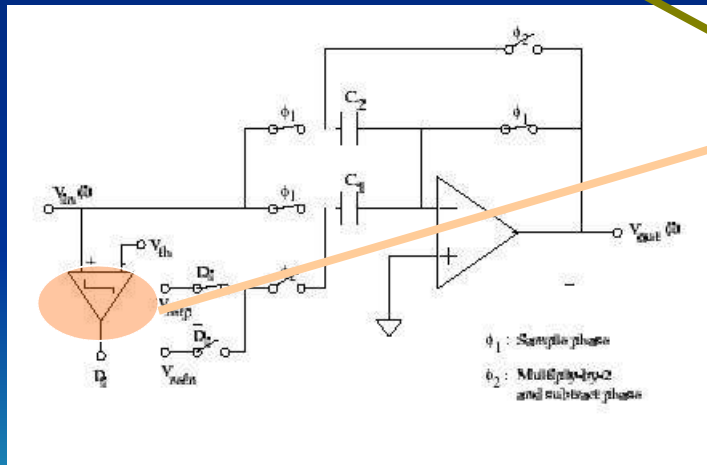- Preamplifier
- Decision circuit
- Output buffer



How to design ...



Case : Pipeline ADC design

- First Step :

 - Architecture Circuit Design

Operational Amplifier

➤ Vdd = 5 V and Vss = - 5V

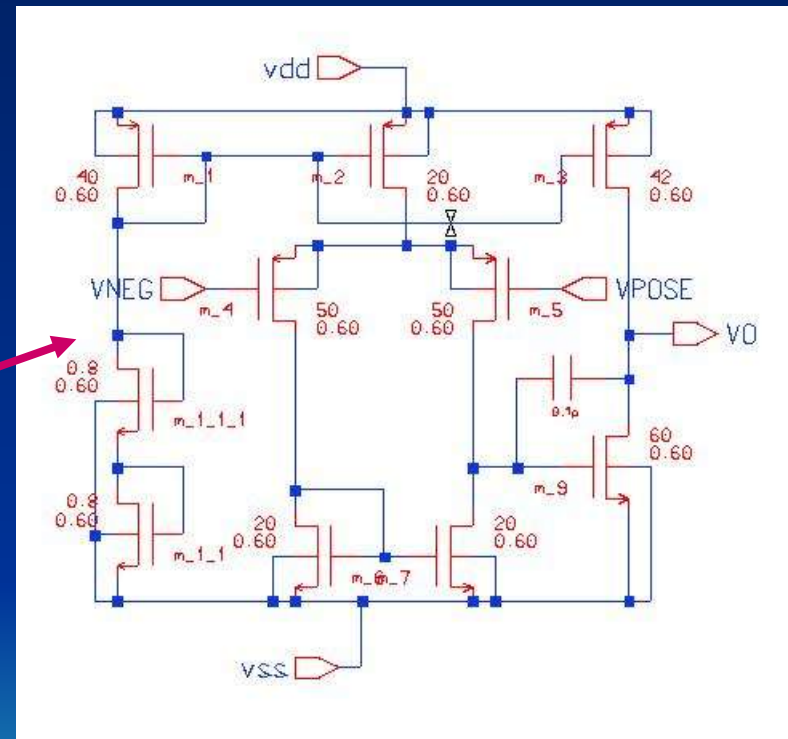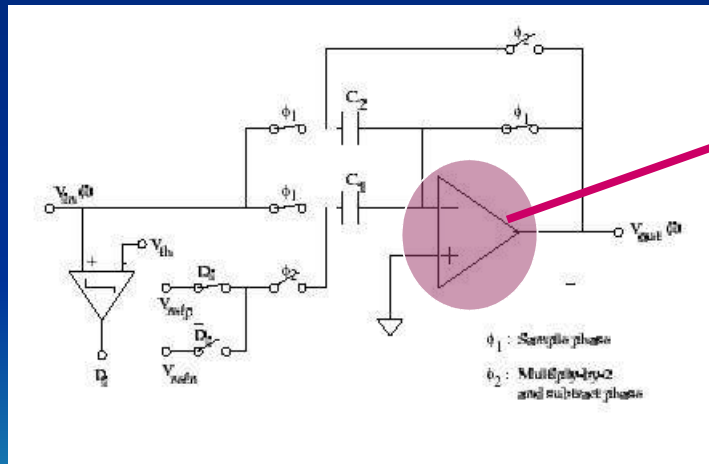

How to design ...

Case : Pipeline ADC design

- Second Step :
 - Done Simulation
 - Result of simulation of Operational Amplifier

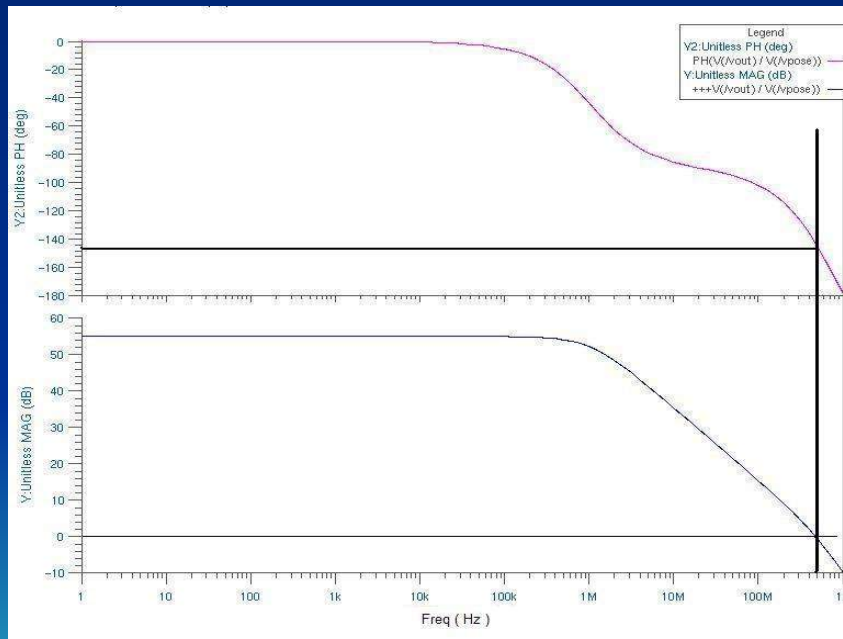



Table 1: OP-Amp Performance

Gain	PM	Gain Bandwidth	Power
55	-145 ^O	800 MHz	10.825 mW

How to design ...

Case : Pipeline ADC design

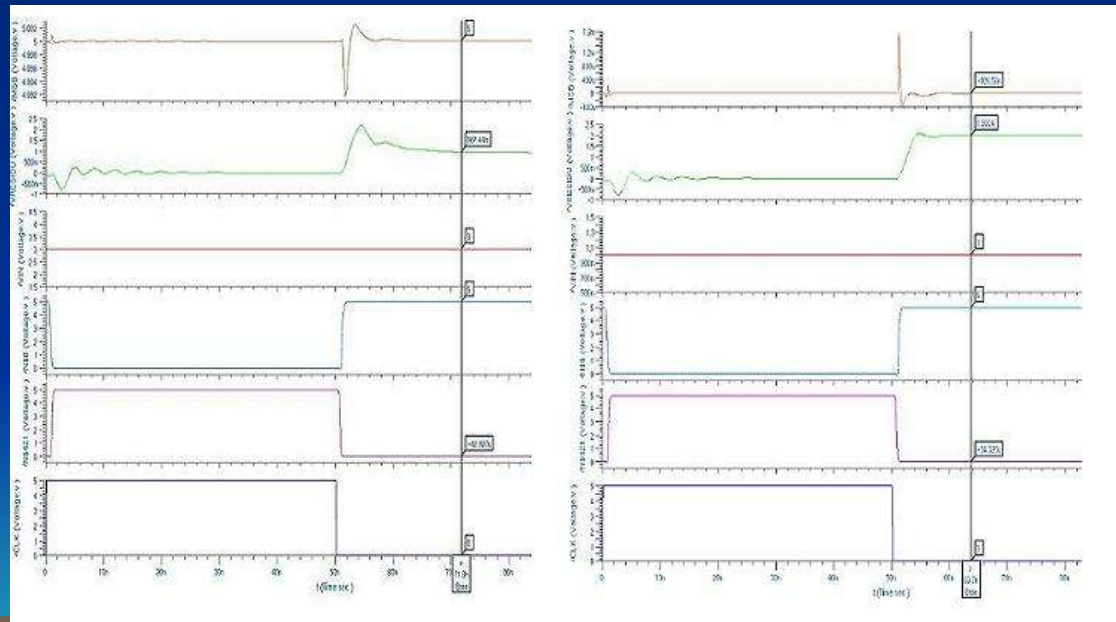
- Second Step :
 - Done Simulation
 - Result of simulation of one bit per stage pipeline



How to design ...

Case : Pipeline ADC design

 
- More Step :
 - Made Layouts
 - One stage A/D converter layout



How to design ...

Case : Pipeline ADC design

 - More Step :
 - Layouts Design
 - 8 bits A/D converter layout



How to design ...

Case : Pipeline ADC design

- More Step :
 - Layouts Design
 - 8 bits ADC layout of CHIP photograph



Sekian

- Terima Kasih
- Thank for your attention
- Merci de votre attention

